



TTL

PRICE
EIGHT SHILLINGS
AND SIXPENCE

**Integrated
logic circuit
applications**
Mullard FJ family

FJ

Integrated Logic Circuit Applications **Mullard FJ Range**

TTL

Made and printed in England
by
WIGHTMAN AND COMPANY LIMITED, 1-3 Brixton Road, London, S.W.9

Industrial Electronics Division
Mullard Limited, Mullard House, Torrington Place, London, W.C.1

The information contained in this book is based on material supplied by B. S. Cowle and J. E. Gilliam of the Mullard Central Application Laboratory.

The issue of the information contained in this publication does not imply any authority or licence for the utilisation of any patented feature.

'Mullard' is the trade mark of Mullard Limited and is registered in most of the principal countries of the world.

© Mullard Limited, 1969
First issued January, 1968
Reprinted with amendments April, 1969

TP963/1

FOREWORD

The Mullard FJ range of integrated circuits uses transistor-transistor logic (TTL). In this book, the characteristics of TTL are explained and, to enable engineers to use the FJ range of TTL integrated circuits to the greatest advantage, numerous application examples are given as well as a great deal of information to assist those engineers who wish to design their own circuits.

CONTENTS

	Page
CHAPTER 1 THE MULLARD FJ RANGE OF TTL INTEGRATED LOGIC CIRCUITS	1
CHAPTER 2 WHAT IS TTL?	3
Introduction: What is TTL? Operation of TTL gate	
CHAPTER 3 HOW TO USE TTL	11
Operating conditions and ratings of the Mullard FJ range of TTL circuits; Using TTL with long transmission lines; Coupling between adjacent signal lines; Effects of supply voltage variations; Hazard conditions in logic systems; Special purpose gates; Bistable elements.	
CHAPTER 4 COMPARATORS	35
Comparators using FJH231; Comparators using AND-OR-NOT gates; Exclusive-OR circuits; Multiple-input comparator	
CHAPTER 5 SHIFT REGISTERS	39
Shift registers using bistable elements; Parallel-input shift registers; Reversible shift registers; Reversible parallel-input shift registers.	
CHAPTER 6 CODE CONVERTERS	47
1248BCD to decimal; Excess-three code to decimal; Gray code to decimal; Johnson code to decimal; Decimal to 1248BCD; Decimal to 1242BCD; Decimal to Aiken code; Decimal to excess-three code; Decimal to Johnson code; Johnson code to 1248BCD; Gray code to 1248BCD; Gray code to binary.	
CHAPTER 7 ERROR DETECTORS	71
1248BCD error detector; Excess-three code error detector; Aiken code error detector; Parity checker.	
CHAPTER 8 ADDERS	79
Half adders; Full adders; Binary adder; Serial adder.	

	Page
CHAPTER 9 COUNTERS	87
Asynchronous and synchronous binary up; Asynchronous and synchronous binary down; Reversible synchronous binary; Synchronous modulo-3 up; Synchronous modulo-5; Synchronous modulo-6; Asynchronous and synchronous 1248BCD up; Asynchronous and synchronous 1248BCD down; Reversible synchronous 1248BCD; Asynchronous 1245BCD up; Excess-three code up; Synchronous Aiken code up; Twisted ring or Johnson code; Synchronous 1248 with cycle length of 12.	
CHAPTER 10 COUNTERS USING THE FJJ141	119
1248BCD decade; Modulo-5; 1245BCD.	
CHAPTER 11 CHAIN CODE GENERATORS	123
Chain code generators with cycle lengths of six, seven, twelve, fifteen, thirty-one, and sixty-three.	
CHAPTER 12 GATED STATICISERS	139
CHAPTER 13 MONOSTABLE CIRCUITS	141
CHAPTER 14 MULTIVIBRATORS	145
CHAPTER 15 LEVEL DETECTORS	149

CHAPTER 1

THE MULLARD FJ RANGE OF TTL INTEGRATED LOGIC CIRCUITS

Several ranges of integrated circuits are available to engineers in the digital applications field. The chief difference between these ranges is in their operating speed, but they also differ in logic levels, power dissipation, supply voltage and in many other respects.

Most applications require devices which operate with propagation delays of the order of 10 to 100ns. These medium-speed devices are used in small and medium-sized computers, peripheral equipment, telephone exchanges, instrumentation and control equipment and in many items of digital equipment associated with telecommunications. In this speed range, two configurations are common—diode-transistor logic (DTL) and transistor-transistor logic (TTL).

The FJ range of integrated logic circuits employs transistor-transistor logic. It conforms to what is becoming a standard TTL configuration in terms of voltage supply, logic levels and pinning. The FJ range is being made in large quantities, resulting in an economic range in which the number of types available is likely to be substantially increased.

The 12ns propagation delay, at 10mW dissipation per gate, of the FJ range is acceptable for most logic applications. However, technological developments will enable compatible ranges in speed and power to be offered alongside the standard range, giving either increased speed or reduced power. All these devices will be available in a dual-in-line outline and, except for the most complex elements, in 14- or 16-lead packs.

An extended temperature range, to military specifications, is also available in the FJ range, with a flatpack outline alternative to the dual-in-line package.

The first part of the range consists of the simpler devices providing a variety of gate functions, bistable circuits, a two-level logic element and an expander element.

The range also contains an ever-increasing number of complex elements performing logic functions such as shift registers, adders and a variety of elements for counting purposes. Because the range is continuously expanding, no type list is included in this book.

CHAPTER 2

WHAT IS TTL?

INTRODUCTION

Electronic logic elements have evolved through a number of stages, beginning with systems consisting of diode AND and OR gates. Advances in semiconductor technology fostered rapid developments in electronic logic circuitry of the active type, and various circuits—such as resistor-transistor logic (RTL), directly-coupled transistor logic (DCTL), diode-transistor logic (DTL) and modified forms of DTL—were produced. The first integrated logic elements were simply translations of discrete component circuits directly into silicon circuits. The earliest types were, in fact, composed of several silicon chips with wire interconnections. As integrated circuit techniques developed, the design approach changed and the circuits began to be designed to suit the manufacturing technology instead of being duplicates of discrete component prototypes. Once it was realised that circuit complexity was not a limiting factor, the way was open to the production of high-performance, complex circuit elements. Transistor-Transistor Logic—TTL—is one product of this philosophy.

WHAT IS TTL?

Integrated circuit techniques allow a number of transistors, diodes and resistors to be made on a single chip of silicon. The various components are then connected to form the required circuit by means of an aluminium interconnection pattern which is deposited on the chip. A cross-section through part of a silicon chip is shown, in diagrammatic form, in Fig. 1 and the plan view of the same chip is shown in Fig. 2. The buried layer is a low-resistivity n-type material compared with the epitaxial n-type layer. This improves the saturation characteristics of the transistor by providing a low resistance path for the collector current.

The TTL gate forms the basis of the complete FJ range of integrated logic circuit elements. The layout of a single TTL gate on a silicon chip is shown in Fig. 3 and the circuit diagram of the gate is shown in Fig. 4. Each transistor lies in a separate isolation region, and all the resistors

share the same isolation area, unless otherwise dictated by layout problems. The epitaxial layer surrounding the resistors is connected to the positive supply, thus reverse-biasing the p-n junction formed between the resistor and the epitaxial layer.

The basic TTL gate is formed by transistors TR_1 and TR_2 as shown in Fig. 4. Transistor TR_1 is a multi-emitter transistor which, together with R_1 , is analogous to the input gate of a DTL circuit, as illustrated in Fig. 5. In the DTL circuit, and for one of the signal paths of the TTL circuit, transistor TR_2 is an inverter transistor. For the other signal path of the TTL gate, TR_2 is an emitter-follower stage. In the DTL gate, TR_2 also serves as the output transistor, whereas in the TTL gate, it is the driver for the push-pull "totem-pole" output stage made up of TR_3 ,

 


Fig. 1—Cross-section through part of a silicon chip

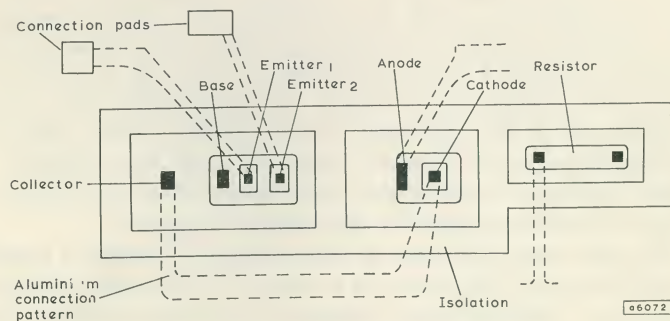


Fig. 2—Plan view of a silicon chip

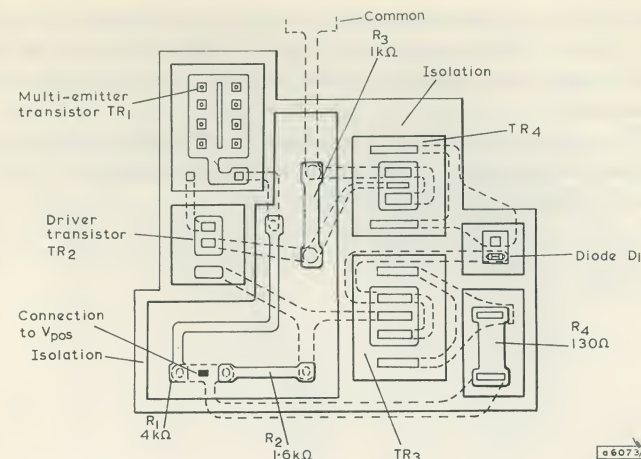


Fig. 3—TTL gate on a silicon chip

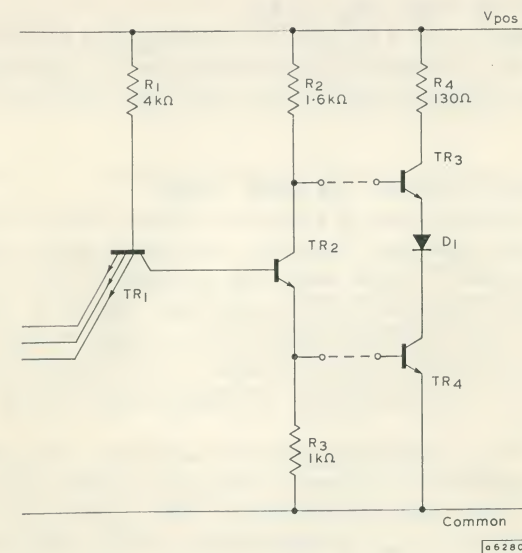


Fig. 4—TTL gate and output stage

TR₄ and D₁ in Fig. 4. Transistor TR₄ is sometimes known as the "pull-up" transistor. In the TTL range, the output stage is used as an interface between the gate and external circuitry, and acts as an inverter in one of the signal paths.

The TTL gate in the FJ range of circuits gives high operating speeds (propagation delay, $t_{pd} = 13\text{ns}$), low power dissipation (10mW) and high logical voltage output ($> 2.4\text{V}$).

In the more complex elements—such as bistable circuits—internal gating functions are performed by that part of the circuit formed by TR₁ and TR₂.

 


Fig. 5—DTL gate

OPERATION OF THE TTL GATE

The explanation of the TTL gate can be simplified by considering the quiescent, or d.c., conditions and switching action separately. The d.c. conditions are considered first for the ON state and then for the OFF state.

D.C. Conditions: ON State—All Inputs "High"

The circuit conditions when all inputs are high are shown in Fig. 6. In the high input state, each input requires a maximum input current, I_{in} , of $40\mu\text{A}$ at the logical '1' input level. The collector of TR₁ is held at the base potential of TR₂; that is, $2V_{BE}$ above zero, say 1.4V . The collector-base diode of TR₁ is forward-biased by the supply voltage via R_1 and the base is therefore at a potential equal to one forward diode voltage drop above the collector potential. The approximate circuit voltages are shown in Fig. 6.

Transistor TR₂ is conducting and is in saturation. The emitter current of TR₂ flows partly in R_3 and partly in the base of TR₄ which is also held in saturation. The voltage at the base of TR₃ is above zero by a value equal to the sum of $V_{CE(sat)}$ of TR₂ and V_{BE} of TR₄. The voltage on the emitter has a value equal to the sum of $V_{CE(sat)}$ of TR₄ and the forward

voltage drop of diode D₁. These voltages are equal, so there is no base drive to TR₃. Transistor TR₃ therefore remains cut off. In this condition, TR₄ can pass a current of 16mA without allowing the logical '0' voltage at the output to exceed 400mV . A typical value for the low-state output voltage at 16mA is 220mV . A current of 16mA is sufficient to drive ten gate inputs in the low state. Somewhat greater output currents may be taken by the gate without damage, but the output voltage rises. This

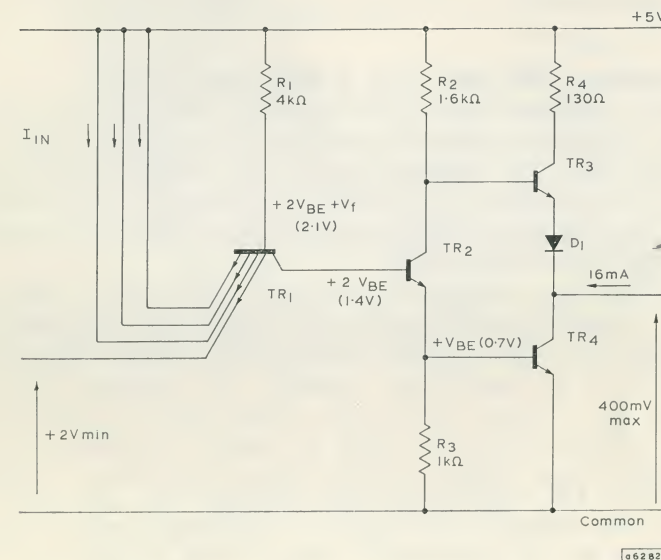


Fig. 6—TTL gate showing the conditions with all inputs high

 


Fig. 7—Typical output characteristic of a TTL gate in the low state

effect is illustrated in Fig. 7. The output resistance in the low state is about 12Ω .

To maintain the circuit in the ON state, the lowest input emitter potential must be sufficiently high to maintain the conditions shown in Fig. 6. The threshold voltage at the input—that is, the input voltage which just causes the output to change state—is about $1.5V$, and therefore, all inputs must be above this level. The test condition used is an input voltage of $+2V$, under which condition an output voltage of less than $0.4V$ at $16mA$ is guaranteed.

D.C. Conditions: OFF State—One or More Inputs “Low”

The circuit conditions for the OFF state are shown in Fig. 8. In this diagram, all the input emitters but one are again shown connected to the positive line. The “low” emitter, however, has a voltage of $800mV$ applied to it in the test conditions. In practice, as explained in the discussion of the ON state, the input voltage can never exceed $400mV$ if it is supplied by the output of a similar circuit.

The current $I_{in(2)}$ consists of two parts— I_b and $I_{in(1)}$. The greater part, I_b , is supplied via R_1 and the emitter-base diode. The smaller part, $I_{in(1)}$, flows as a result of lateral transistor action which occurs between the emitters of the multi-emitter transistor. The maximum total input current, $I_{in(2)}$, is $1.6mA$, and thus the output current of $16mA$ of a gate in the ON state is sufficient to supply ten inputs. The collector of TR_1 is at a voltage $V_{CE(sat)}$ above the input voltage. This voltage is insufficient to turn both TR_2 and TR_4 on fully, although TR_2 may, in the test condition with $800mV$ at the input, be conducting slightly. Transistor TR_4 remains cut off. The collector voltage of TR_2 is high, and TR_3 is, therefore, turned on. Under the conditions stated, the output voltage, with an output of $400\mu A$, which is the input current of ten gates in the high state, is guaranteed to be not less than $2.4V$. With an input voltage of less than $800mV$, a typical value for the output voltage is $3.3V$.

A typical output characteristic of a gate in the high state is shown in Fig. 9. The output current into a short circuit has a minimum value of $18mA$ and a maximum value of $58mA$. The current is limited by R_4 and, to some extent, by D_1 . In a multiple gate, not more than one output must be connected to the “common” line at any one time, since damage may be caused due to excessive dissipation. The output resistance of the circuit is typically 100Ω in the high state.

A typical transfer characteristic of the TTL gate is shown in Fig. 10. In the high state, if a current greater than the normal maximum of $400\mu A$ is taken, the output voltage begins to fall.

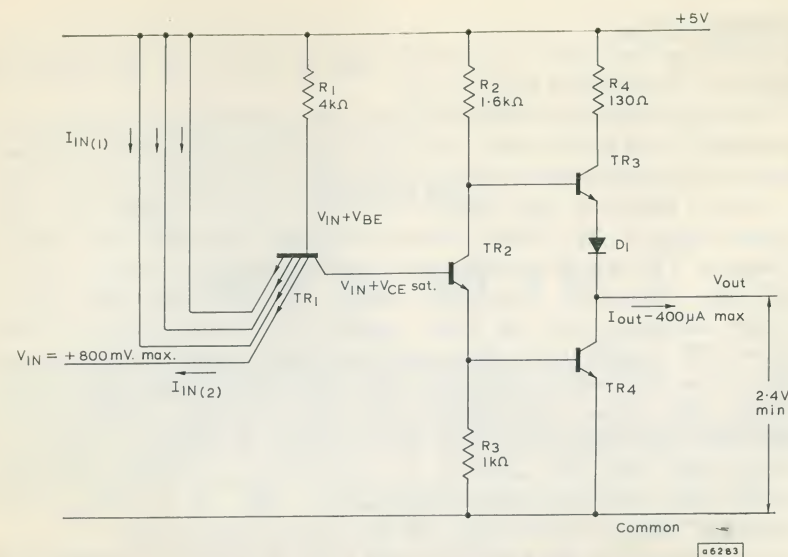


Fig. 8—TTL gate showing the conditions in the OFF state

 


Fig. 9—Typical output characteristic of a TTL gate in the high state

Switching Action

In switching from the '1', or OFF, state to the '0', or ON, state, the sequence of operations is as follows:

One input is assumed to be initially at zero potential and the others are connected to the positive line. The high inputs have a current flowing into them, as discussed earlier, and the current flowing out from the low input is about 1.6mA. As the voltage of the low input is raised, the input current begins to fall. When the input reaches about 0.8V, the collector voltage of TR_2 is 0.8V plus $V_{CE(sat)}$ and TR_2 begins to conduct, and its collector voltage falls. The output voltage, therefore, also falls and this process continues until the input reaches the threshold value of about 1.4 or 1.5V. At this point, the output has fallen to about 2V. The base of TR_2 is now at a voltage of about 1.4V, and both TR_2 and TR_4 are conducting. The output falls rapidly to the value of $V_{CE(sat)}$ of TR_4 . At the same time, TR_2 is saturated, and TR_3 is turned off. There is a short time during which both TR_3 and TR_4 are conducting, and during this time a current flows from the positive line, via R_4 , TR_3 , D_1 and TR_4 , to the "common" line.

In switching from the low to the high state, the inputs are initially high. As the voltage of one or more inputs is reduced to a value of about 1.4V, the collector voltage of TR_1 falls below the voltage required to hold both TR_2 and TR_4 in conduction. The current in TR_2 falls, and the collector voltage rises, turning TR_3 on. The output then rises to a logical '1' level.

If the gate is used with a capacitive load of 15pF, typical values for the propagation delay are 8ns to set a logical '0' and 18ns to set a logical '1'. The total value of t_{pd} is, therefore, $(8+18)/2$, which is equal to 13ns. The low output impedance in both states allows the TTL gate to drive capacitive loads effectively, and an increase from 15 to 150pF in the capacitive load produces an increase in typical propagation delay from 13ns to about 23ns. The short propagation delay and the ability to drive capacitive loads are the two most important advantages of TTL. They make TTL suitable for applications where a clock frequency of 4MHz is required and where cable connections give rise to capacitive loads.

CHAPTER 3

HOW TO USE TTL

OPERATING CONDITIONS AND RATINGS OF THE MULLARD FJ RANGE OF TTL CIRCUITS

A summary of the most important data for the FJ range of TTL circuits is given in Table 1.

TABLE 1

Summarised data for the FJ range of TTL circuits

Absolute maximum supply voltage	7V
Operating supply voltage	4.75 to 5.25 V
Absolute maximum input voltage	5.5V
Maximum input current requirements:	
"low" state (measured at $V_{in} = 0.4V$)	-1.6mA per input
"high" state (measured at $V_{in} = 2.4V$)	+40µA per input
Fan-out over full operating temperature range:	
for gates	10
for buffer gates	30
for expanders	3
Temperature range for commercial types:	
operating	0 to +70°C
storage	-55 to +150°C
Temperature range for military types:	
operating	-55 to +125°C
storage	-65 to +150°C

Noise Margin

Each gate has, associated with it, two d.c. noise margins—one for the high input state and the other for the low input state. These margins may be quoted in relation to typical values or worst-case values of logic level and transfer characteristic.

The 'typical' noise margins may be defined by reference to the typical transfer characteristic shown in Fig. 10. The gates are assumed to be

operating at full fan-out and the temperature is assumed to be 25°C. The high state noise margin at the input to gate Y is the difference between the typical logical '1' level from gate X and the value of V_{in} associated with the value of V_{out} for gate Y which gives a maximum logical '0' level. From the figures given on Fig. 10, this value can be calculated as $3.3 - 1.4$, which is equal to 1.9V.

The low-state noise margin is the difference between the typical value of logical '0' level from gate X and the value of V_{in} associated with the value

 


Fig. 10—Typical transfer characteristic of a TTL gate

of V_{out} for gate Y which gives a minimum logical '1' level. Again, numerical values can be obtained from Fig. 10 giving a value of noise margin of $1.2 - 0.2$, or 1V.

The 'worst-case' noise margins may also be defined by considering Fig. 10. These noise margins are based on the assumptions that the gates are operating at full fan-out over the full temperature range and that the transfer characteristic is the worst possible. The worst possible transfer characteristic passes through points A and B in Fig. 10. In the high input state, the minimum logical '1' level acceptable from gate X is 2.4V, and the worst-case transfer characteristic gives an input threshold value of 2V for a maximum value of logical '0' at the output of gate Y. The high-state noise margin is therefore $2.4 - 2$, or 0.4V. In the low state, the maximum value of logical '0' acceptable from the gate X is 0.4V, and for a minimum value of logical '1' at the output of gate Y, the worst-case transfer characteristic gives an input value of 0.8V. The low-state noise margin is therefore $0.8 - 0.4$, or 0.4V.

Supply-line and "Common"-line Noise

Any "common"-line noise appears at the gate output in the low state. In the high state the output is isolated from this noise source.

Noise on the supply line is fed via R_2 and TR_3 to the output in the high state. In the low state this noise source has no effect.

When circuits of the FJ range are used, it is advisable, if long supply leads are used, to decouple the supply leads by means of a capacitor of about 10nF or greater.

Noise Coupled to Signal Lines

Because of the low output impedance of the gate in either the high or the low state, noise coupled to signal lines has no effect except when very long signal paths are used.

Power Dissipation

The supply current to a normal TTL gate at a supply level of 5V and with a logical '0' at the output has a typical value of 3mA. With a logical '1' at the output, the current required is 1mA in the unloaded condition.

The total power dissipation with a 1:1 duty ratio is therefore $(5 \times 3 + 5 \times 1)/2$ or 10mW. The dissipation is increased slightly with loading and pulse repetition frequency as shown in Fig. 11.

 


Fig. 11—Typical variation in dissipation with loading and frequency

Unused Inputs

Unused gate inputs may be left open-circuit, connected to a positive supply of between 2.4 and 5.5V or connected in parallel with a driven input of the same gate. Leaving inputs open-circuit, however, can give

rise to unwanted pick-up. Pick-up noise can be eliminated by connecting unused inputs to a positive supply, and this connection also gives slightly faster gate operation than leaving the unused inputs open-circuit.

The fastest and safest method of dealing with unused gate inputs is to connect them in parallel with used inputs. This method prevents pick-up noise, eliminates the danger of over-voltage at the input caused by supply voltage variations, and gives an improvement in speed of between 0.5 and 1 μ s per paralleled input.

Unused \bar{J} and \bar{K} inputs *MUST* be connected to the "common" line.

USING TTL WITH LONG TRANSMISSION LINES

In a self-contained logic system, logic elements are usually connected together by short wires or by printed wiring connections. However, it is sometimes necessary to connect circuits which are separated by a distance of tens of metres; for instance, when connections are required between circuits mounted on different racks. When long interconnections are needed, they must be effected by means of transmission lines to preserve the pulse edges and to prevent noise pick-up. These lines may be coaxial or twisted-pair transmission lines. The lines used in practice normally have a characteristic impedance of between 50 and 100 Ω and, when these lines are used, the gates must have a high input impedance and a low output impedance. These lines, which have a velocity ratio between 0.7 and 0.9, introduce delays into the system. Where this delay is less than the switching time of the gate, the effects of the line need not be considered. This is so for lines up to 30cm long because the delay for a 30cm line is approximately 1ns.

However, with longer lines, delays of about 5ns/m are common. These delays can be explained by studying Fig. 12 and the equivalent circuits for transition and d.c. states shown in Fig. 13. Gate 1 drives gate 2 directly, and gate 3 via a transmission line. The open-circuit voltage of gate 1 is E volts and is fed from a source resistor $R_{S(1)}$. The input resistances of gates 2 and 3 are termed $R_{L(2)}$ and $R_{L(3)}$ respectively, and the line has a characteristic impedance Z_0 .

There are three conditions to be considered with different relative magnitudes for line impedance and gate input and output impedances. The first condition is when $R_{L(2)}$ and $R_{L(3)}$ are low compared with Z_0 , and $R_{S(1)}$ is high. The second is when the impedances are matched and the third is when $R_{L(2)}$ and $R_{L(3)}$ are high compared with Z_0 , and $R_{S(1)}$ is low.

For the first condition, when gate 1 switches, the instantaneous voltage at the input to the line is some fraction of E , the actual value being determined by $R_{S(1)}$, $R_{L(2)}$ and Z_0 which act as a resistive divider network.

For the amplitude of this initial voltage to be sufficient to act as a logical '1' at gate 2, the value of E must be much higher than the gate input threshold voltage. Apart from the difficulty of generating high voltage logical signals, the noise margin of such a system would be very poor. When the signal travels down the line to gate 3, it is reflected in

 


Fig. 12—Gates connected by a long transmission line

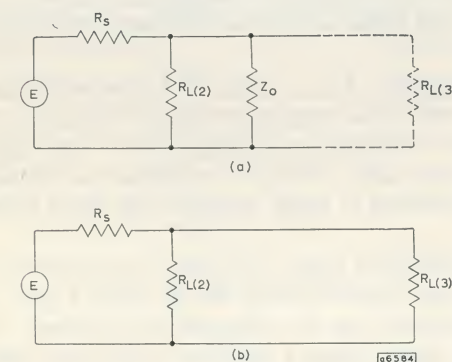


Fig. 13—Equivalent circuit of transmission line connection of gates

- (a) during switching transient
- (b) under static conditions

antiphase, because Z_0 is greater than $R_{L(3)}$, subtracting from the initial signal but still leaving a signal great enough to switch gate 3. Had the signal been reflected in phase, it would have added to the initial signal and so assisted gate 2 to turn on.

With input, output and line impedances as described above, a satisfactory logic system cannot be designed. No fan-out is possible, since

loading extra gates on the output of gate 1 only reduces the signal levels. Much of the above argument applies equally to matched input, output and lines impedances, where useful fan-out cannot be obtained without a very high source e.m.f. or, more precisely, a high ratio between source e.m.f. and input threshold voltage. Reflections do not occur in a matched system, but if more than one gate of impedance Z_0 is connected to the line output, a mismatched condition is set up.

The next condition to consider is that in which $R_{S(1)}$ is low compared with the line impedance and the input resistances, $R_{L(2)}$ and $R_{L(3)}$, are very much higher than the line impedance. When gate 1 switches, the initial voltage level at the input to the line is approximately $E Z_0 / (R_{S(1)} + Z_0)$. This voltage is high enough to exceed the threshold level of gate 2 immediately, and gate 2 switches. The signal then travels down the line and, after a period of one line delay, gate 3 switches. The termination presented by $R_{L(3)}$ is almost the same as an open-circuit and the signal is therefore reflected at double the amplitude. On reaching the input to the line, the reflected signal meets a low impedance, and the excess charge in the line is dissipated in this low impedance. During this process a number of small reflections occur, but these are not of sufficient amplitude to be of any consequence.

The output impedance, $R_{S(1)}$, of the TTL gate in the low state is 10 to 12 Ω . In the high state it has a typical value of 70 Ω and a maximum value of 100 Ω . The input impedance in the high state is very high—of the order of 100k Ω . In the low state, the input impedance is normally about 4k Ω , but if the input potential is made negative, the input impedance falls to about 500 Ω .

The waveforms obtained when TTL gates are used with a 50 Ω cable as shown in Fig. 12 are shown in Fig. 14. In Fig. 14, gate delays are not shown. The waveforms may be interpreted as follows. At the positive edge of the input signal, gate 1 switches to the low state. The output impedance of gate 1 is low and the line input voltage immediately falls to the logical low level, switching gate 2. A wavefront travels down the line until it arrives, after a period of one line delay, at gate 3. The input impedance appears to be an open-circuit termination on the line, and the wavefront is reflected at twice the original amplitude (t_1). Gate 3 switches. The reflected wave travels back down the line, reaching gate 1 at t_2 and attempts to cause a negative voltage step at the input to the line. The output impedance of gate 1 is, however, low and therefore the incident wave is attenuated and reflected with a phase reversal. The effect of this is to produce a small negative voltage step at t_2 .

After two more line delays, this step has travelled down the line and back and is attenuated once again at the input to the line (t_3).

When the input signal falls at the end of the input pulse (t_4), gate 1 switches off, but, since its output impedance in the high state can be as high as 100 Ω , the rise in voltage at the input to the line is attenuated to a value $V_H Z_0 / (Z_0 + Z_G)$, where V_H is the high-state output voltage of gate 1, Z_0 is the characteristic impedance of the line and Z_G is the gate output impedance in the high state. This initial step is insufficient to switch gate 2. A wave now travels down the line and is reflected in phase (t_5). At t_6 the reflected wave reaches the beginning of the line and a signal level of sufficient amplitude to switch gate 2 is established. The output pulse at gate 2 is, therefore, delayed by a period equal to two line delays.

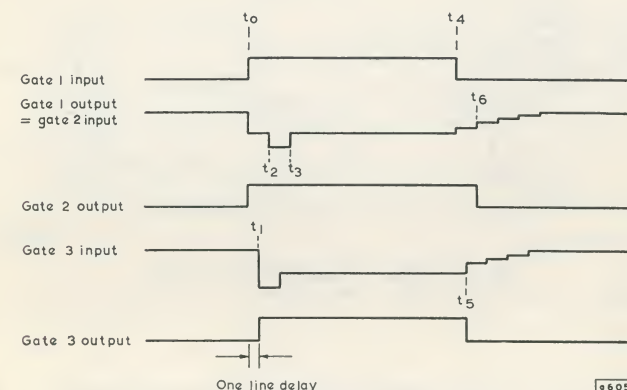


Fig. 14—Waveforms with 50 Ω line

When low impedance lines—for instance, 50 Ω —are used, or when the loading at the input to the line is heavy, the gates connected to the input of the line may not switch until the second reflection occurs.

If an 80 Ω line is used and typical values for E and $R_{S(1)}$ are assumed to be 3.5V and 70 Ω respectively, a triggering potential of 1.9V is available which is just greater than the threshold potential of gate 2, which therefore switches at time t_4 . Operation under these conditions is, therefore, possible but the threshold potential is exceeded by such a small margin that reliable operation cannot be guaranteed.

The best method of improving the situation is to use a buffer gate to drive an 80 Ω line. This method ensures reliable triggering even under extremely bad conditions.

COUPLING BETWEEN ADJACENT SIGNAL LINES

A connection using a length of twin cable is shown in Fig. 15. Since the conductors are parallel to each other, capacitive coupling exists between them. The waveforms obtained when switch S_1 is open—that is, when gate 2 is in the low state—are shown in Fig. 16. When gate 1 switches, an overswing appears on the waveform at C due to reflections in the line. Because of the low impedance presented by the output of gate 2, the voltage coupled to the other line is very small—some tens of millivolts. No effect is observed at F.

 


Fig. 15—Gates connected by twin pair

 


Fig. 16—Waveforms obtained with switch S_1 of Fig. 15 open

The waveforms obtained when switch S_1 is closed—that is, when gate 2 is in the high state—are shown in Fig. 17. With S_1 closed, capacitively-coupled negative-going edges are conducted away by the output impedance of gate 2. When this occurs, the line becomes charged, the capacitively-coupled signal becomes positive and the voltage at B is raised. The diode

in the totem-pole output is now reverse-biased and the line is discharged by the leakage current of the output stage and the reverse input current of the multi-emitter transistor of the driven gate. Therefore, a new d.c. level is established on the line and on the output of gate 2.

With a high pulse repetition frequency—higher than about 1MHz—the waveform at B and D does not have time to decay, and the negative level only falls to about 3.5 or 4V, which is well above the minimum logical '1' level. Gate 2, therefore, does not switch.

 


Fig. 17—Waveforms obtained with switch S_1 of Fig. 15 closed

With a pulse repetition frequency so low that the line discharges via the various leakage resistances between pulses, the negative-going edge capacitively-coupled to B is conducted away by the low output impedance of gate 2. Again, gate 4 is not affected.

EFFECTS OF SUPPLY VOLTAGE VARIATIONS

The performance of TTL gates as quoted in published data is guaranteed over a supply voltage range from 4.75 to 5.25V. Supply voltage variations outside this range affect both fan-out and, to a lesser extent, speed.

The effects on the d.c. output conditions at 25°C are shown for the high state in Fig. 18 and for the low state in Fig. 19. From these figures it can be seen that, as the supply voltage is increased, the fan-out capability increases.

The effect on propagation delay is shown in Fig. 20 for fan-outs of 1 and 10. From this graph it can be seen that as the supply voltage is increased, the propagation delay decreases slightly.

 


Fig. 18—Typical variation in output characteristic with variation in supply voltage in the high state

 


Fig. 19—Typical variation in output characteristic with variation in supply voltage in the low state

 


Fig. 20—Variation in propagation delay with variation in supply voltage

HAZARD CONDITIONS IN LOGIC SYSTEMS

In some systems it is possible for "race" conditions to develop because of differences in propagation delays and in signal path lengths. For example, two supposedly identical systems could be built, in each of which two signals from separate sources are fed to a common gate. In one system, signal A might arrive before signal B, whereas in the other system, signal B might arrive first, resulting in a different logical action being performed. This type of condition can occur in closed loop systems such as d.c.-coupled bistable elements.

In a bistable circuit used as a triggered element, the new state of the internal gates depends upon the previous state. Whilst the previous state information is necessary to determine the new state, this information must also be destroyed in setting up the new state. In edge-triggered d.c.-coupled bistable elements, this information is sometimes stored only for the duration of one or two gate propagation delays and it is possible that, when a very slow transition from one state to the other is made, the stored information will be lost or confused. This can also result from race conditions outside the bistable element.

When the two edge-triggered elements in the FJ range are used, a maximum clock pulse rise time of 150ns prevents the occurrence of this kind of race condition hazard.

 


Fig. 21—Shift register using J-K bistable elements

When a number of bistable elements are connected together, a different kind of race condition may occur. For instance, a shift register using J-K bistable elements is shown in Fig. 21. At each clock pulse, the information held in the shift register is required to shift one place to the right. In the argument which follows, the threshold voltage level at which stage 2 triggers is assumed to be lower than that of the other stages. The threshold voltages of stages 0, 1, 2 and 3 are known as $V_{TH(0)}$, $V_{TH(1)}$, $V_{TH(2)}$ and $V_{TH(3)}$ respectively. If, initially, the state of the shift register is 0101 and a further '0' is shifted into stage 0 at the clock pulse, the shift register

should assume the state 0010. However, if a slowly rising edge is applied to the clock line, when $V_{TH(2)}$ is reached, stage 2 sets to '1' and later, when $V_{TH(0)}$, $V_{TH(1)}$ and $V_{TH(3)}$ are reached, these three stages operate according to the input information present at the time. In the example being considered, the final state of the register would be 0011.

This condition can only occur if the clock pulse transition time from $V_{TH \min}$ to $V_{TH \max}$ is longer than the sum of the minimum propagation delay and the minimum set-up time of the bistable element. The clock pulse should, ideally, pass through $V_{TH \min}$ to $V_{TH \max}$ in less than 15ns in circuits where hazard conditions could arise.

This requirement indicates a clock ramp rate of about 50mV/ns for the FJJ131 and 30mV/ns for the FJJ101. These figures, which are based on worst-case temperature conditions, correspond to clock pulse rise times of approximately 35ns for the FJJ131 and 60ns for the FJJ101. For operation at uniform temperature, maximum clock pulse rise times of 50 and 100ns respectively are recommended for the two devices.

Transient Hazards

Transient hazard conditions can occur when, for instance, gates are connected as shown in Fig. 22, and signals A and B change state simultaneously in opposite directions. This results in both inputs to gate 3 being above the threshold voltage for a short time which, in turn, results in the generation of an output pulse of very short duration. This effect is illustrated in Fig. 23. In some circumstances, the generation of this unwanted pulse can cause unpredictable errors.

A hazard condition could arise where each of the two gate inputs is fed from the Q output of a bistable element when the two bistable elements are fed from a common clock pulse. The propagation delay to set '1' in the bistable element might be as much as 50ns and as little as 10ns, whilst the propagation delay to set '0' might lie between 10 and 35ns.

 


Fig. 22—Connection which may give rise to transient hazards

 


Fig. 23—Waveforms illustrating transient hazards

If one of the bistable elements were fast and the other were slow, the overlap at the input to the gate could be 25ns in one direction and -40ns in the other. This could cause an output pulse from the gate of 25ns duration for one transition and no pulse from the other transition. A 25ns pulse is sufficient to set a bistable element connected to the output of the gate.

The situation is aggravated when one of the signals to gate 3 is supplied from a gate with passive pull-up, as shown in Fig. 24. In these circumstances, the delay in changing from a '0' to a '1' is longer, resulting in the effect illustrated in Fig. 25. From this diagram, it can be seen that the first unwanted negative-going pulse, at point E, is narrow because it is generated in the way described above, but the second unwanted pulse is much

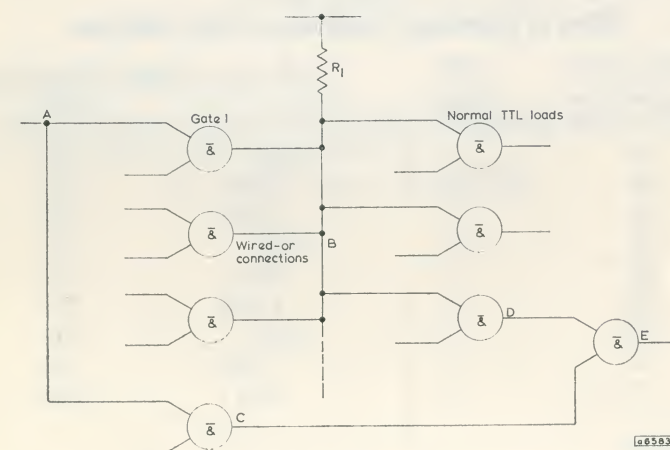


Fig. 24—Connection which may give rise to more severe transient hazards

 


Fig. 25—Waveforms illustrating severe transient hazards

longer because of the delay in the gate with passive pull-up. This pulse may be above the threshold voltage for a period of several nanoseconds.

The severity of the hazard depends upon the exact operating conditions of the circuit. There are several variables which must be considered. The value of propagation delay of gate 1 depends on the value of resistor R_1 and on the capacitive loading. Both of these values are determined by the number of wired-OR connections at B and the number of normal TTL loads at B. Examples of the duration of the pulse at E are given in Table 2 for an output pulse of amplitude 4V. The use of the lowest possible resistor value reduces the error pulse width and gives the greatest operating speed but increases the power dissipation.

TABLE 2
Effect of Operating Conditions on Pulse Duration

Wired-OR Connections	TTL Loads	R	Output Pulse Duration (ns)
0	1	330Ω	11
0	1	1kΩ	20
0	1	4.7kΩ	26
0	5	330Ω	13
0	5	1kΩ	25
0	5	4.7kΩ	28
7	1	330Ω	20
7	1	1.2kΩ	35
7	7	1kΩ	30

Timing Problems encountered when using Edge-triggered and Master-Slave Bistable Elements

Logic signals in a system are frequently derived from bistable elements, processed by a number of gating stages and, finally, stored in a second group of bistable elements. If the sending and receiving bistable elements are either both of the master-slave type or both of the edge-triggered type, only the timing problems already discussed are likely to arise. If the sending bistable element is of the master-slave type and the receiving bistable element is of the edge-triggered type, the behaviour of the system is predictable although not always immediately obvious. If, however, the sending element is of the edge-triggered type and the receiving element is of the master-slave type, the behaviour of the system is unpredictable because the J and K signals to the receiving element are derived at the

leading edge of the clock pulse, which is the time when the master-slave element is reading J and K information in. The J and K information at the receiving element may be incorrectly registered. This type of connection is, therefore, undesirable and should be avoided if possible.

SPECIAL-PURPOSE GATES

The FJ range of TTL integrated circuits contains three types of special-purpose gate:

- FJH151 Dual AND-OR-NOT gate
- FJH171 Quadruple AND-OR-NOT gate
- FJH231 Quadruple two-input gate without pull-up transistor, for wired-OR use

FJH151 Dual AND-OR-NOT Gate

The circuit diagram of the FJH151 dual AND-OR-NOT gate is shown in Fig. 26. The output of this gate is given by:

$$(\bar{A} + \bar{B}).(\bar{C} + \bar{D}) \text{ or } \overline{A.B + C.D}$$

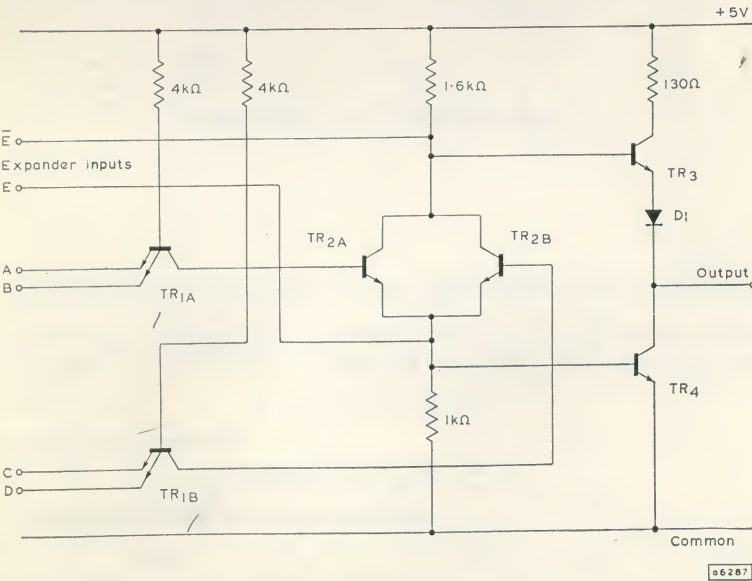


Fig. 26—AND-OR-NOT gate

The FJH151 gate can be expanded by means of the FJY101 which is shown in Fig. 27.

If the expander inputs are used, the output becomes:

$$\overline{A.B+C.D+E_1+E_2+E_3\dots}$$

where E_1, E_2, E_3 are the outputs of expanders 1, 2, 3 respectively and, in general, $E = a.b.c.d.$

Not more than four FJY101 expanders may be connected to one FJH151.

This gate may be used to provide the exclusive-OR function or as an equality gate in a comparator. The necessary inputs are shown in Fig. 28.

 


Fig. 27—One gate of the FJY101 element

 


Fig. 28—Use of the AND-OR-NOT gate type FJH151

FJH171 Quadruple AND-OR-NOT Gate

The circuit diagram of the FJH171 quadruple AND-OR-NOT gate is shown in Fig. 29. The output of this gate is given by:

$$\overline{A.B+C.D+E.F+G.H}$$

Expander, or node, inputs are provided for use with the expander FJY101. If the expander inputs are used the output becomes:

$$\overline{A.B+C.D+E.F+G.H+E_1+E_2+E_3\dots}$$

where E_1, E_2, E_3 are the outputs of expanders 1, 2, 3 respectively and, in general, $E = a.b.c.d.$

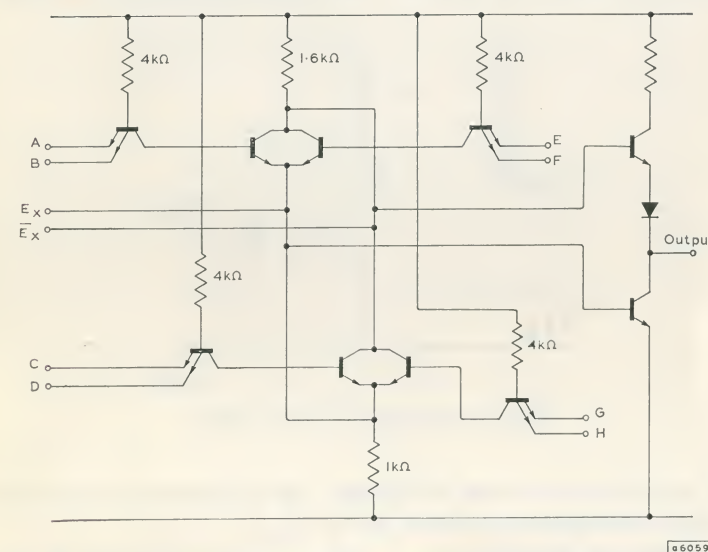


Fig. 29—Circuit diagram of the quadruple AND-OR-NOT gate type FJH171

If the expander inputs are neglected, the gate can perform a double exclusive-OR function. This is achieved by feeding the gate inputs with

$$A.B, \bar{A}.B, C.D, \bar{C}.D$$

The output then becomes

$$(A.B + \bar{A}.B).(C.D + \bar{C}.D)$$

If the inputs are fed with the functions

$$A.B, \bar{A}.B, C.D, \bar{C}.D$$

the output is

$$(A.B + \bar{A}.B).(C.D + \bar{C}.D)$$

which is the required output for a two-stage comparator. This function would normally be written

$$(A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (A_2 \cdot B_2 + \bar{A}_2 \cdot \bar{B}_2)$$

where A_1 , A_2 and B_1 , B_2 are the quantities being compared.

FJH231 Quadruple Wired-OR Gate

The FJH231 is similar to the FJH131 but without the isolation diode and pull-up transistor. The circuit diagram of the FJH231 is given in Fig. 30. The load resistor is provided externally by the user, and with the proper choice of this resistor for any particular application, gates may be connected together to perform the wired-OR function and still be

 


Fig. 30—One section of the FJH231

capable of driving up to nine TTL loads. The connections to perform the basic wired-OR function are shown in Fig. 31.

If the inputs are fed with

$$A \cdot \bar{B}, \bar{A} \cdot B,$$

the output becomes

$$A \cdot B + \bar{A} \cdot \bar{B},$$

and if the inputs are fed with

$$A \cdot B, \bar{A} \cdot \bar{B},$$

the output is

$$A \cdot \bar{B} + \bar{A} \cdot B.$$

It is evident, therefore, that the gate performs a similar function to the FJH151 dual AND-OR-NOT gate.

The wired-OR function may be expanded to provide a similar function to the FJH171 as shown in Fig. 32.

 


Fig. 31—Wired-OR connection

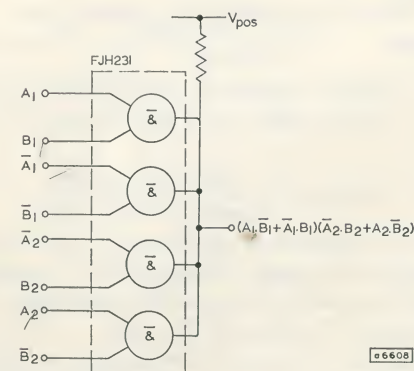
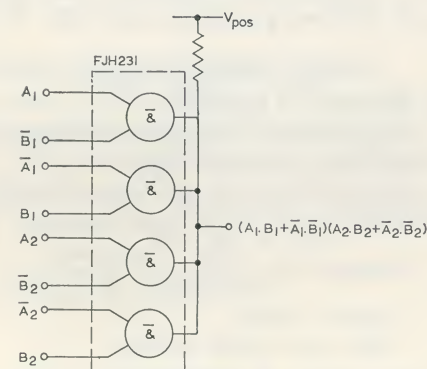


Fig. 32—Wired-OR connection of more than two gates

The switching speeds associated with a resistive pull-up are similar to those of a normal TTL gate when switching from '1' to '0', but the transition from '0' to '1' is slower because output and circuit capacitances must be charged via the load resistor. Minimum rise times are achieved by using a low value of collector resistor, but since this increases the collector current of the output transistor, less current is available for driving other loads.

Increasing the value of collector resistor to give a higher fan-out decreases the operating speed as already explained, but it also introduces an additional difficulty; namely, that when other TTL gates are being driven, the high-state input current of these gates must not cause the output voltage of the driving gate to fall below the minimum logical '1' level.

To calculate the maximum and minimum permitted values for the load resistor, R_L , the following equations are used. The load current, I_L , is given by:

$$I_L = NI_{in(H)} + PI_{out}$$

where N = fan-out to TTL loads
 $I_{in(H)}$ = input current of a gate in the high state
 P = fan-out to wired-OR loads
 I_{out} = leakage current of the output transistors

Therefore, the maximum value of the load resistance, R_L , is given by:

$$R_{Lmax} = \frac{V_{pos} - V_{out(H)min}}{NI_{in(H)max} + PI_{outmax}}$$

where V_{pos} = supply voltage
 $V_{out(H)}$ = high state output voltage

The maximum total current to be supplied by the output transistor, I_{totmax} , is given by:

$$I_{totmax} = \frac{V_{pos} - V_{out(L)max}}{R_{Lmin}} + NI_{in(L)max}$$

where $V_{out(L)}$ = output voltage of a gate in the low state
 $I_{in(L)}$ = input current of a gate in the low state

Therefore

$$R_{Lmin} = \frac{V_{pos} - V_{out(L)max}}{I_{totmax} - NI_{in(L)max}}$$

In the low state, the maximum output current that can be taken without exceeding the guaranteed output voltage of 0.4V is 16mA and this is the value which should be used for I_{tot} in the calculation. The chosen load resistor must lie between R_{Lmin} and R_{Lmax} .

It is possible to connect as many as seven gates by the wired-OR method and still maintain a fan-out of seven into TTL loads. Five wired-OR connections allow the fan-out to be increased to eight and two gates

connected by the wired-OR method allow a fan-out of nine.

When the FJH231 is used to drive only TTL loads and a 4kΩ collector resistor is used, a fan-out of ten is available.

The minimum value of supply voltage should be used in the calculation of R_{Lmax} , and the maximum value should be used to calculate R_{Lmin} .

BISTABLE ELEMENTS

The FJ range of TTL integrated circuits contains three types of bistable element:

FJJ111, FJJ121	Master-slave J-K bistable element
FJJ101	Edge-triggered J-K bistable element
FJJ131	D bistable element

FJJ111, FJJ121 Master-slave J-K Bistable Element

The single master-slave bistable element, FJJ111, has three J and three K inputs. It has a maximum operating frequency of at least 10MHz but typically 15MHz. The truth table of the J-K bistable element is given in Table 3. In this table, Q_{n+1} and \bar{Q}_{n+1} are the states at the Q and \bar{Q} outputs after the action of a clock pulse. The functions performed at the J and K inputs are $J = J_1.J_2.J_3$ and $K = K_1.K_2.K_3$.

The "preset" and "clear" terminals set the state of the Q and \bar{Q} independently of the clock input.

TABLE 3

Truth Tables of J-K Bistable Element

J	K	Q_{n+1}	\bar{Q}_{n+1}
0	0	Q_n	\bar{Q}_n
1	0	1	0
0	1	0	1
1	1	\bar{Q}_n	Q_n
Preset	Clear	Q_{n+1}	\bar{Q}_{n+1}
0	0	1	1
1	0	0	1
0	1	1	0
1	1	Q_n	\bar{Q}_n

A waveform diagram illustrating the operation of the J-K bistable element is given in Fig. 33. Before the clock pulse arrives, the element is shown in the '0' state. At time t_1 , the master circuit is disconnected from the slave. This occurs when the clock voltage reaches about 1V. At time t_2 , information is read in from the J and K inputs to the master circuit. This occurs when the clock input reaches a level of approximately 2V. At time t_3 , the input AND gates are disconnected from the master circuit, and at time t_4 , the master information is transferred to the slave circuit. After the propagation delay, the appropriate voltage levels appear at the output terminals.

 


Fig. 33—Operation of master-slave bistable element with $J = '1'$ and $K = '0'$

The clock pulse duration must be at least 20ns, and the J and K information must be held static during the clock pulse and for a total time of at least 25ns. Changes of J and K information during the clock pulse may cause the output to set accordingly. Typical values for propagation delay are 26ns to set '0' and 34ns to set '1'.

The preset, clock and clear inputs each represent two TTL loads while the J and K inputs represent one load each. The fan-out from the bistable element as with the other TTL elements is 10 from each output. The supply current required is 8mA, corresponding to a dissipation of 40mW.

The FJJ121 is a dual version of the master-slave element which has only single J and K inputs to each bistable circuit.

FJJ101 Edge-triggered J-K Bistable Element

The logic diagram of the FJJ101 edge-triggered J-K bistable element is given in Fig. 34. The element operates at a frequency of at least 20MHz and typically up to 35MHz. The element is provided with multiple J and K inputs but, unlike the master-slave elements, the FJJ101 has two direct inputs to each of the J and K AND gates, and one input to each of these gates via an inverter. The logic functions performed at the J and K inputs are, therefore, $J = J_1 \cdot J_2 \cdot \bar{J}^*$ and $K = K_1 \cdot K_2 \cdot \bar{K}^*$.

In the edge-triggered bistable element, the input information is transferred to the output on the leading, or positive-going, edge of the clock

pulse. Typical values of propagation delay are 27ns to set '1' and 18ns to set '0'. The time taken to read in the J and K information is known as the "set-up" time and has a maximum value of 20ns. This time occurs before the clock pulse reaches the threshold value. After the clock pulse threshold value has been reached, the input information must remain for 5ns. This is known as the "hold" time. The J and K information must therefore be present at least 20ns before the clock pulse threshold and must remain for 5ns after it. After this time, J and K information is locked out and can have no further effect on the state of the bistable element until the clock pulse is discontinued.

In the bistable element, the clock pulse leading edge must rise to the logical '1' level in less than 150ns. Slower rates of rise than this introduce the possibility of race conditions which could cause an erroneous output as described under the heading "Hazard Conditions in Logic Systems".

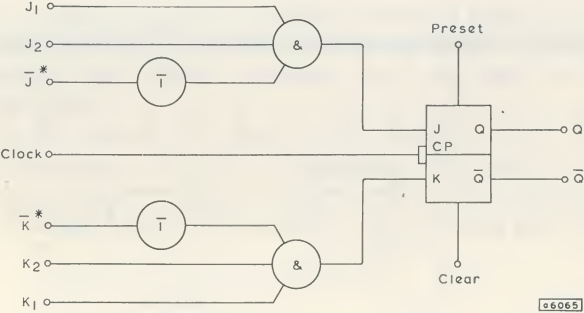


Fig. 34—Edge-triggered J-K bistable element type FJJ101

FJJ131 Dual D Bistable Element

The D bistable element is a delay element which delays information between input and output by one clock period. The truth table for a D bistable element is given in Table 4. The states shown are those after the leading edge of the clock pulse.

TABLE 4
Truth Table for D Bistable Element

D	Q_{n+1}
0	0
1	1

The D bistable element may be used as a triggered element if \bar{Q} is connected to D as shown in Fig. 35. The FJJ131 is also provided with "preset" and "clear" inputs.

The operating frequency is at least 15MHz and typically 25MHz. The set-up and hold times have maximum values of 20ns and 5ns respectively and a clock pulse rise time of not more than 150ns is required. The waveform diagram given in Fig. 36 shows the typical propagation delays of 28ns to set '1' and 20ns to set '0'. The maximum values for these delays are 35ns and 50ns respectively.

 


Fig. 35—D bistable element connected as a T bistable element

 


Fig. 36—Waveforms of D bistable element

CHAPTER 4

COMPARATORS

Comparators are used to determine whether two binary numbers are equal. For two single-bit numbers A and B to be equal, the required function is

$$A \cdot B + \bar{A} \cdot \bar{B}$$

This can be achieved by the use of an AND-OR-NOT gate or by connecting two NAND gates by the wired-OR method as explained in Chapter 3.

To compare two multi-bit numbers A_0 to A_n and B_0 to B_n , the required function is

$$(A_0 \cdot B_0 + \bar{A}_0 \cdot \bar{B}_0) \cdot (A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (A_2 \cdot B_2 + \bar{A}_2 \cdot \bar{B}_2) \cdots (A_n \cdot B_n + \bar{A}_n \cdot \bar{B}_n)$$

When comparators are used in conjunction with counters, the complements of the signals are usually available as well as the signals themselves, but if the complements are not available, they must be generated.

COMPARATORS USING FJH231

 


Fig. 37—One-bit comparator using FJH231

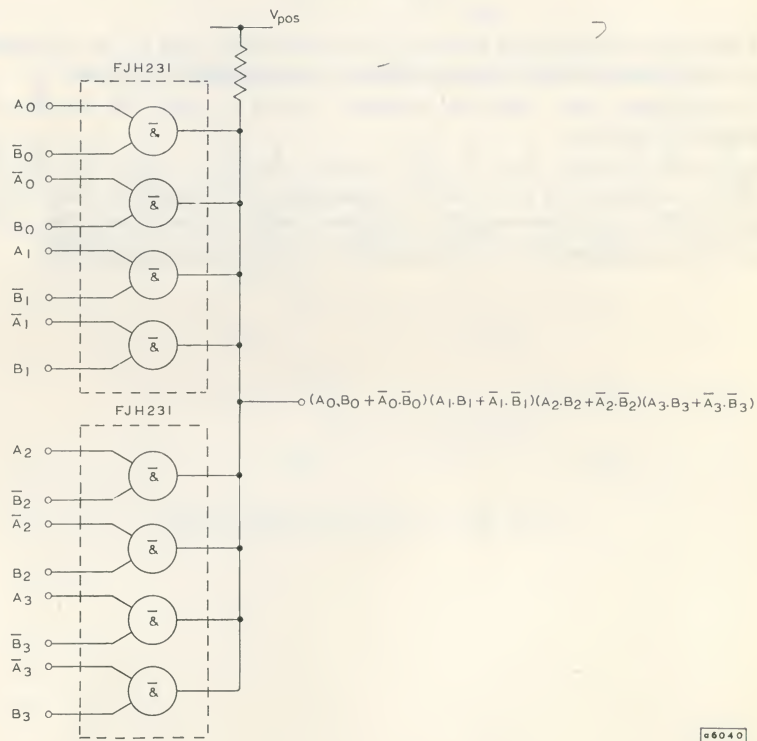


Fig. 38—Four-bit binary comparator for use as a BCD comparator

COMPARATORS USING AND-OR-NOT GATES

 


Fig. 39—One-bit comparator using an AND-OR-NOT gate

 


Fig. 40—Two-bit comparator using a quadruple AND-OR-NOT gate

EXCLUSIVE-OR CIRCUITS

 


Fig. 41—Exclusive-OR circuit using an AND-OR-NOT gate

 


Fig. 42—Exclusive-OR circuit using NAND gates

MULTIPLE-BIT COMPARATOR

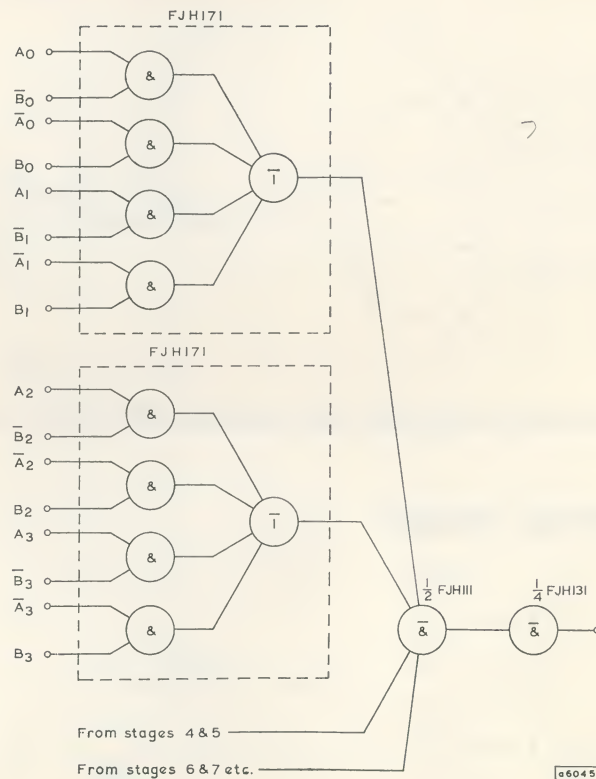


Fig. 43—Multiple-bit comparator using NAND and quadruple AND-OR-NOT gates

CHAPTER 5

SHIFT REGISTERS

A shift register shifts the contents of one bistable element in a series into the next when a “shift” pulse is received. If the contents are shifted into the following bistable element, the shift register is said to be forward-shifting but if the contents are shifted into the preceding bistable element, the shift register is said to be reverse-shifting. A reversible shift register has its stage interconnections changed from forward to reverse, or vice-versa, by gates.

Shift registers are the basis of stores, sequence control units, chain code generators and some counters. Shift registers may either be built to accept information sequentially or in parallel. Bistable elements of the D or J-K types are suitable for use in shift registers but, when edge-triggered bistable circuits are used, the clock pulse rise times must be short enough to preclude the occurrence of any interstage hazard conditions as explained in Chapter 3.

Where wired-OR connections using the FJH231 are used, the value of the pull-up resistor may need to be changed if further loads are added. The method of selecting a suitable value has already been explained in Chapter 3.

SHIFT REGISTERS USING BISTABLE ELEMENTS

 


Fig. 44—Shift register using dual D bistable elements

 


Fig. 45—Shift register using dual J-K bistable elements

PARALLEL-INPUT SHIFT REGISTERS

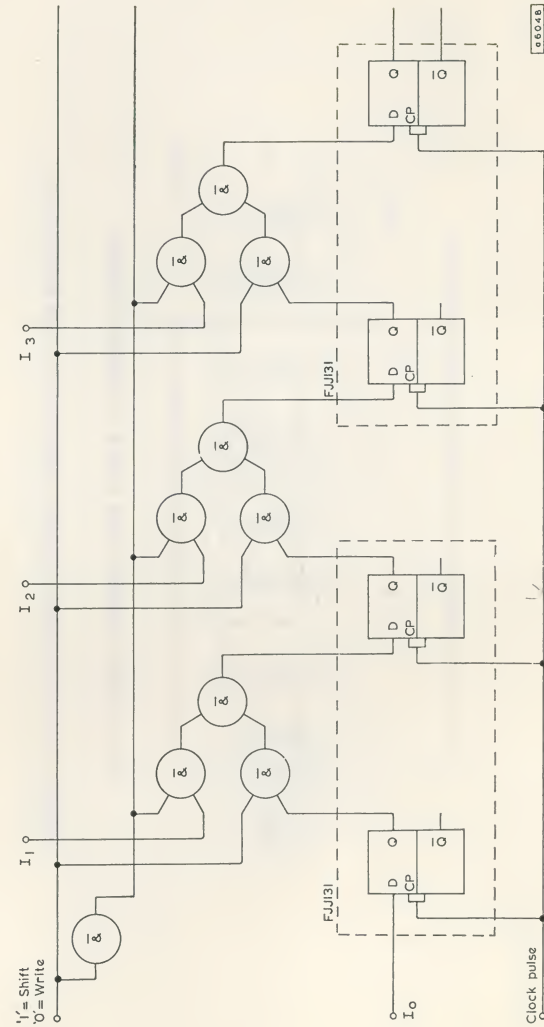


Fig. 46—Parallel-input shift register using dual D bistable elements and NAND gates


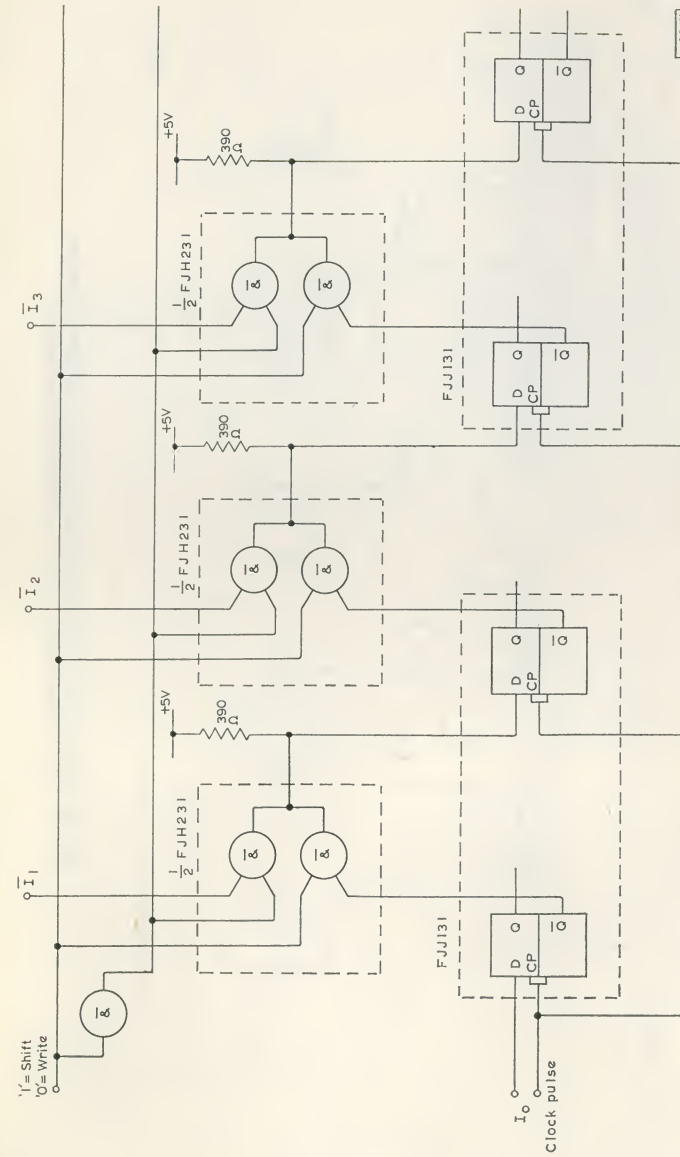



Fig. 47—Parallel-input shift register using dual D bistable elements and NAND gates with the wired-OR connection

REVERSIBLE SHIFT REGISTERS

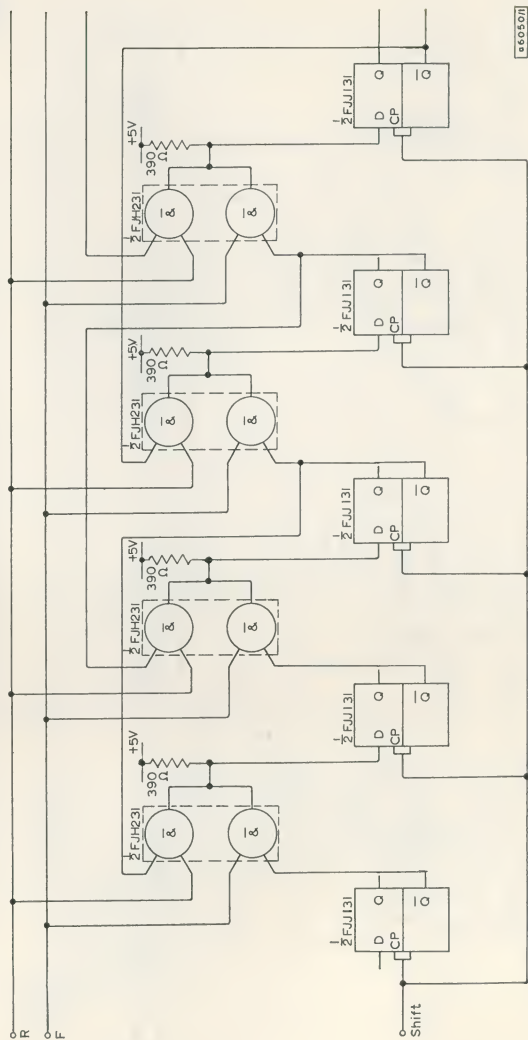

660501

Fig. 48—Reversible shift register using dual D bistable elements and NAND gates with the wired-OR connection

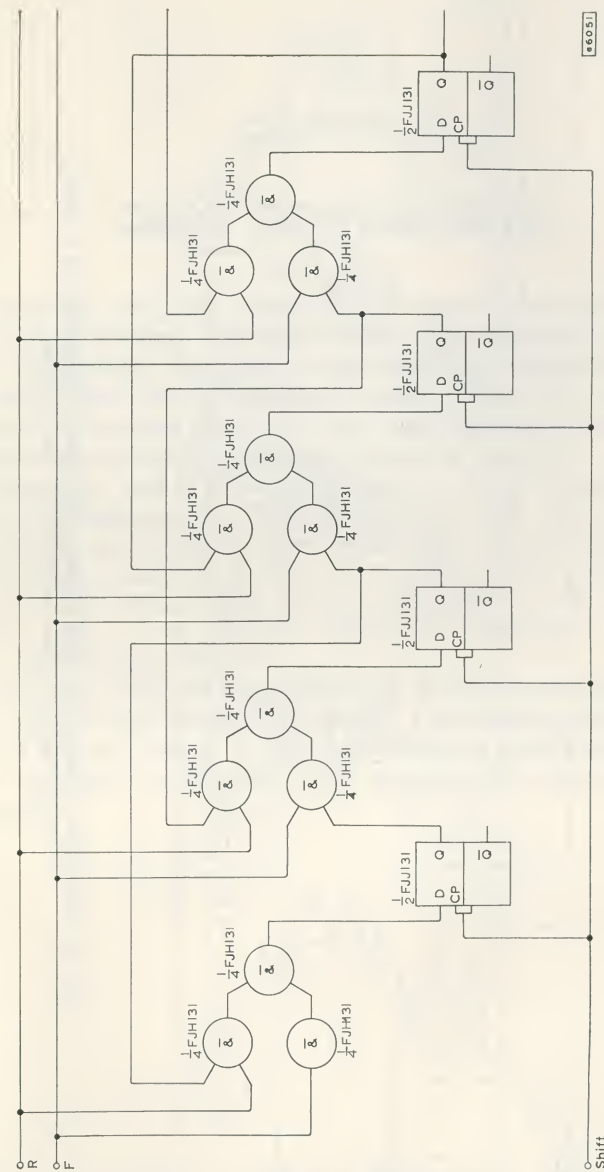

660511

Fig. 49—Reversible shift register using dual D bistable elements and NAND gates

REVERSIBLE PARALLEL-INPUT SHIFT REGISTER

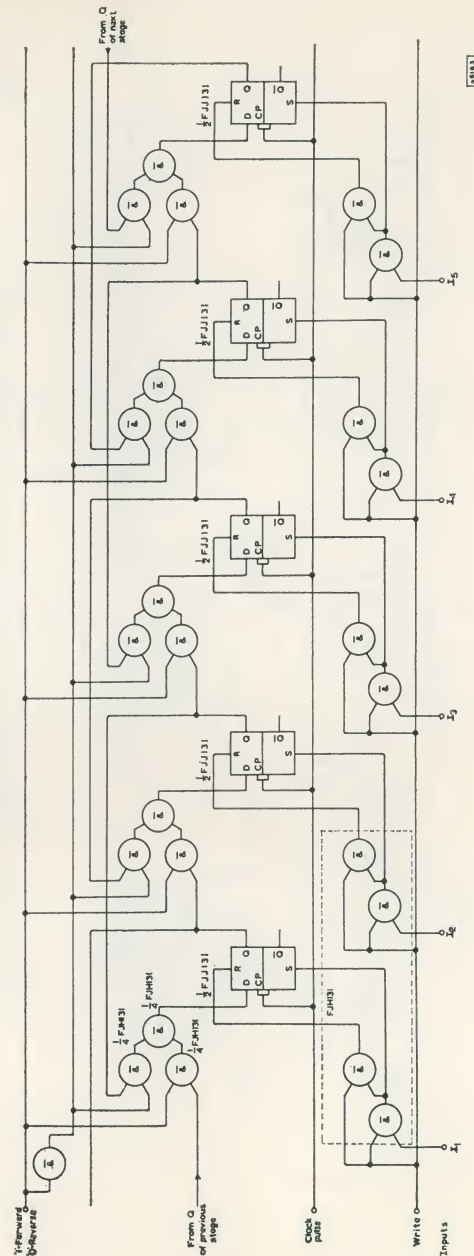


Fig. 50—Reversible parallel-input shift register with inputs independent of a clock, using dual D bistable elements and NAND gates

CHAPTER 6

CODE CONVERTERS

Code converters are gating systems which convert information from one coded form to another. The most common code converters are used to convert information from binary-coded-decimal, excess-three code or some other coded form into decimal numbers. These code converters are also known as decoders. Code converters which convert decimal numbers into some coded form are sometimes known as encoders.

In some codes, such as binary-coded-decimal, not all the possible states are used; for instance, in 1248BCD the states 1010, 1011, 1100, 1101, 1110 and 1111 are not used. These unused states are known as redundancies and their existence enables the number of gate inputs of code converters to be reduced. This method of simplifying code converters is explained fully in the Mullard publication "Electronic Counting—Circuits, Techniques, Devices"*.

Resistors are shown on converters with decimal inputs because these may be supplied from mechanical switches. The resistors ensure that open inputs are held at a logical '1' level and reduce the possibility of pick-up. If these converters are fed from other gating circuits, the resistors may be omitted.

*Cowle, B. S. and Gilliam, J. E., "Electronic Counting—Circuits, Techniques, Devices", Mullard Limited, October, 1967.

1248BCD TO DECIMAL CONVERTER

All outputs are high except the energised number

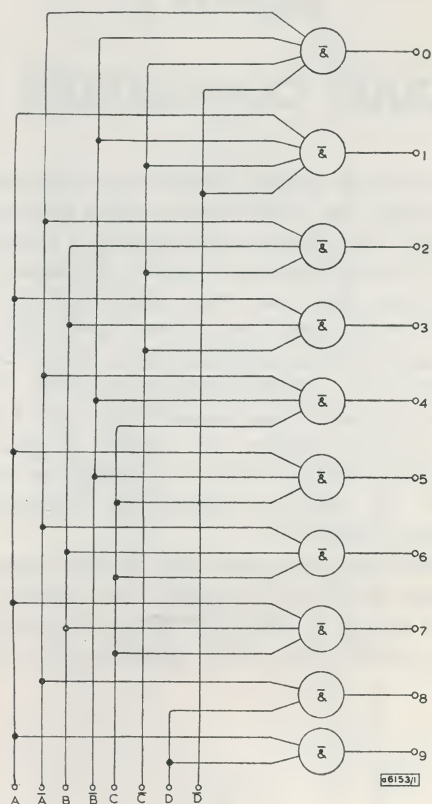


Fig. 51—1248BCD to decimal converter

Truth Table

	D Weight = 8	C 4	B 2	A 1	Simplification
0	0	0	0	0	$\bar{A}.\bar{B}.\bar{C}.\bar{D}$
1	0	0	0	1	$A.\bar{B}.\bar{C}.\bar{D}$
2	0	0	1	0	$\bar{A}.B.\bar{C}$
3	0	0	1	1	$A.B.\bar{C}$
4	0	1	0	0	$\bar{A}.\bar{B}.C$
5	0	1	0	1	$A.\bar{B}.C$
6	0	1	1	0	$\bar{A}.B.C$
7	0	1	1	1	$A.B.C$
8	1	0	0	0	$\bar{A}.D$
9	1	0	0	1	$A.D$

1248BCD TO DECIMAL CONVERTERS AND NUMERICAL INDICATOR TUBE DRIVERS

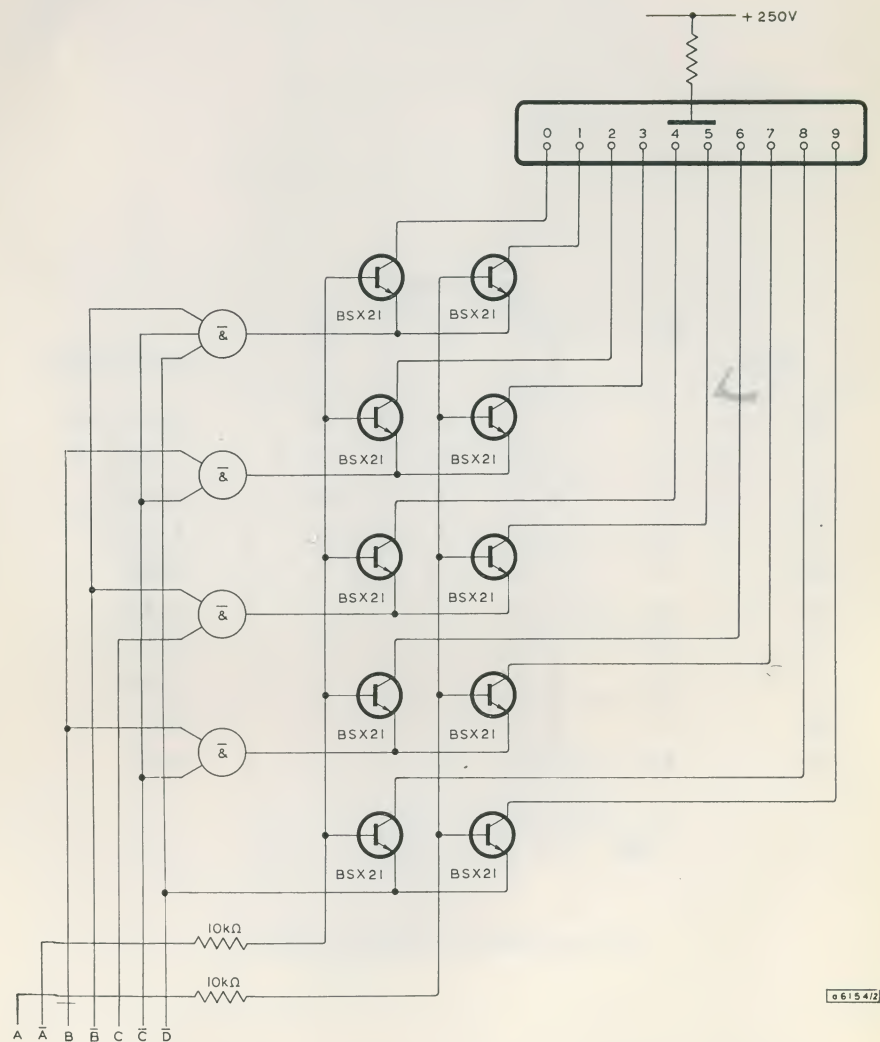


Fig. 52—1248BCD to decimal converter and numerical indicator tube driver

 


Fig. 53—1248BCD to decimal converter and numerical indicator tube driver using FJL101

Truth Table					
	D	C	B	A	
	Weight = 8	4	2	1	Simplification
0	0	0	0	0	$\bar{A}.\bar{B}.\bar{C}.\bar{D}$
1	0	0	0	1	$A.\bar{B}.\bar{C}.\bar{D}$
2	0	0	1	0	$\bar{A}.B.\bar{C}$
3	0	0	1	1	$A.B.\bar{C}$
4	0	1	0	0	$\bar{A}.\bar{B}.C$
5	0	1	0	1	$A.\bar{B}.C$
6	0	1	1	0	$\bar{A}.B.C$
7	0	1	1	1	$A.B.C$
8	1	0	0	0	$\bar{A}.D$
9	1	0	0	1	$A.D$

EXCESS-THREE CODE TO DECIMAL CONVERTER

All outputs are high except the energised number

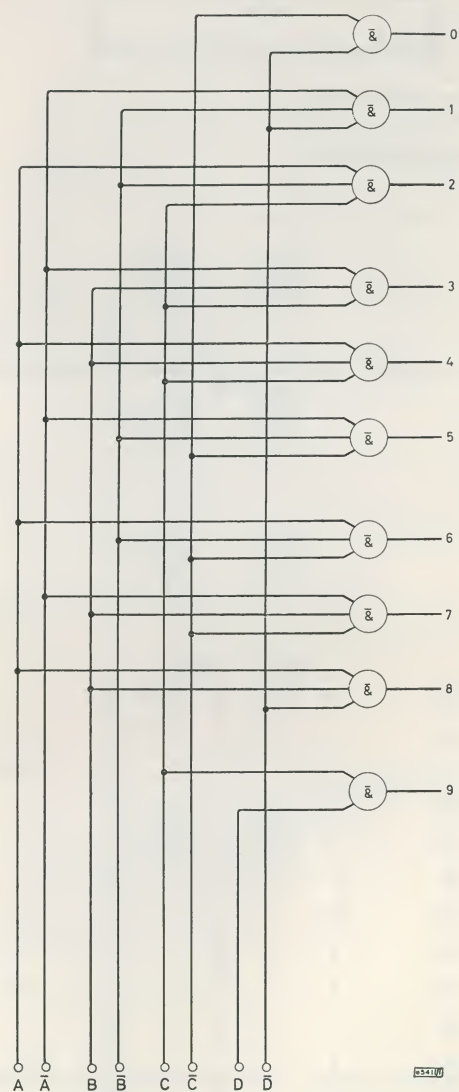


Fig. 54—Excess-three code to decimal converter

Truth Table

	D	C	B	A	Simplification
0	0	0	1	1	$\bar{C}.D$
1	0	1	0	0	$\bar{A}.\bar{B}.\bar{D}$
2	0	1	0	1	$A.\bar{B}.C$
3	0	1	1	0	$\bar{A}.B.C$
4	0	1	1	1	$A.B.C$
5	1	0	0	0	$\bar{A}.\bar{B}.\bar{C}$
6	1	0	0	1	$A.\bar{B}.\bar{C}$
7	1	0	1	0	$\bar{A}.B.\bar{C}$
8	1	0	1	1	$A.B.D$
9	1	1	0	0	$C.D$

GRAY CODE TO DECIMAL CONVERTER

Gray code with a cycle length of 10

All outputs are high except the energised number

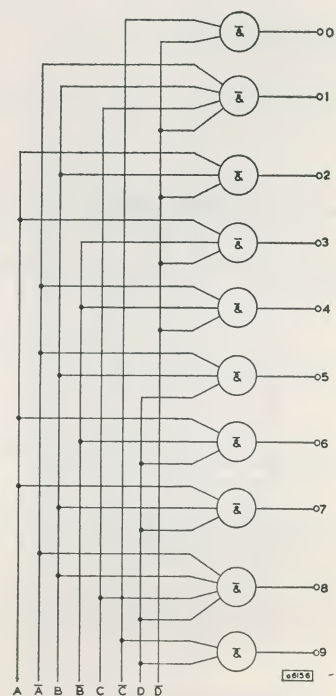


Fig. 55—Gray code to decimal converter

Truth Table

	D	C	B	A
0	0	0	1	0
1	0	1	1	0
2	0	1	1	1
3	0	1	0	1
4	0	1	0	0
5	1	1	0	0
6	1	1	0	1
7	1	1	1	1
8	1	1	1	0
9	1	0	1	0

JOHNSON CODE TO DECIMAL CONVERTER

All outputs are high except the energised number

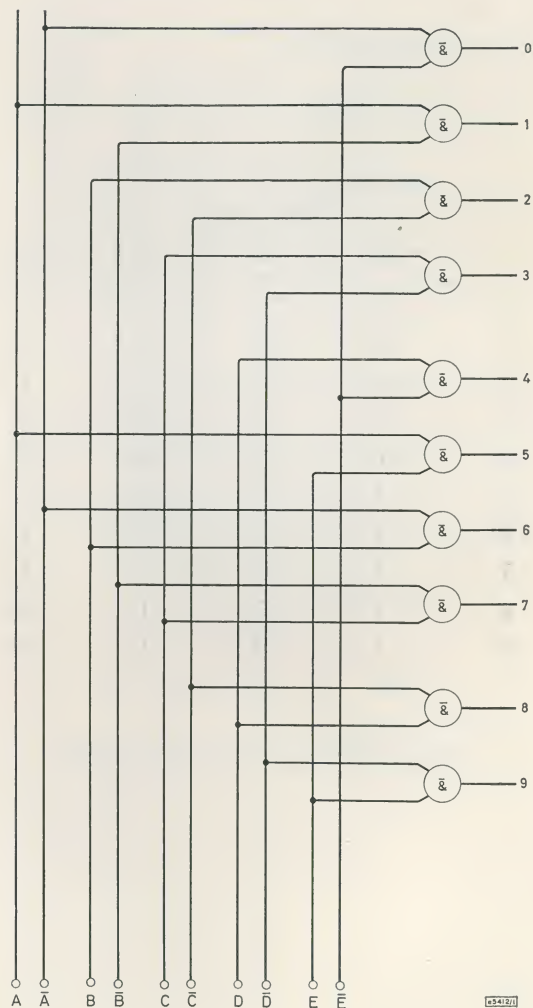


Fig. 56—Johnson code to decimal converter

Truth Table

	E	D	C	B	A	Simplification
0	0	0	0	0	0	$\bar{A}.\bar{E}$
1	0	0	0	0	1	$A.\bar{B}$
2	0	0	0	1	1	$B.\bar{C}$
3	0	0	1	1	1	$C.\bar{D}$
4	0	1	1	1	1	$D.\bar{E}$
5	1	1	1	1	1	$A.E$
6	1	1	1	1	0	$\bar{A}.B$
7	1	1	1	0	0	$\bar{B}.C$
8	1	1	0	0	0	$\bar{C}.D$
9	1	0	0	0	0	$\bar{D}.E$

DECIMAL TO 1248BCD CONVERTER

All inputs are high except the energised number

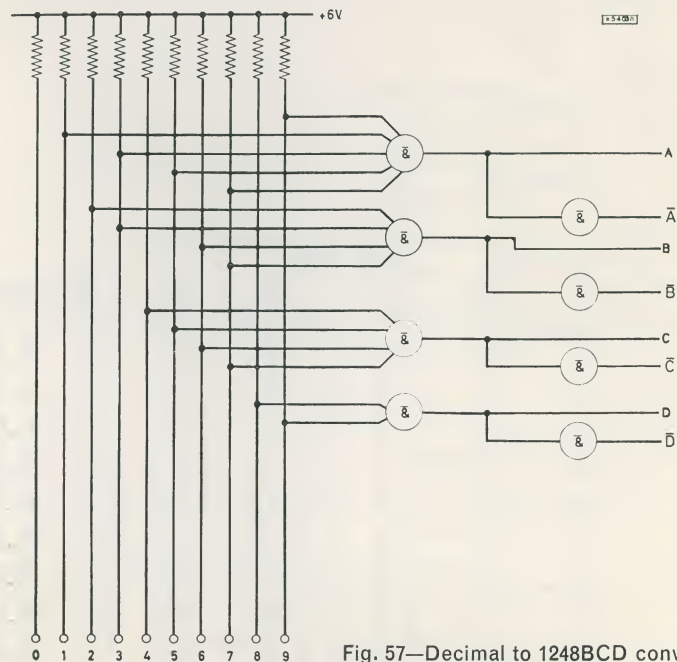


Fig. 57—Decimal to 1248BCD converter

Truth Table

	D Weight = 8	C 4	B 2	A 1
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

DECIMAL TO 1242BCD CONVERTER

All inputs are high except the energised number

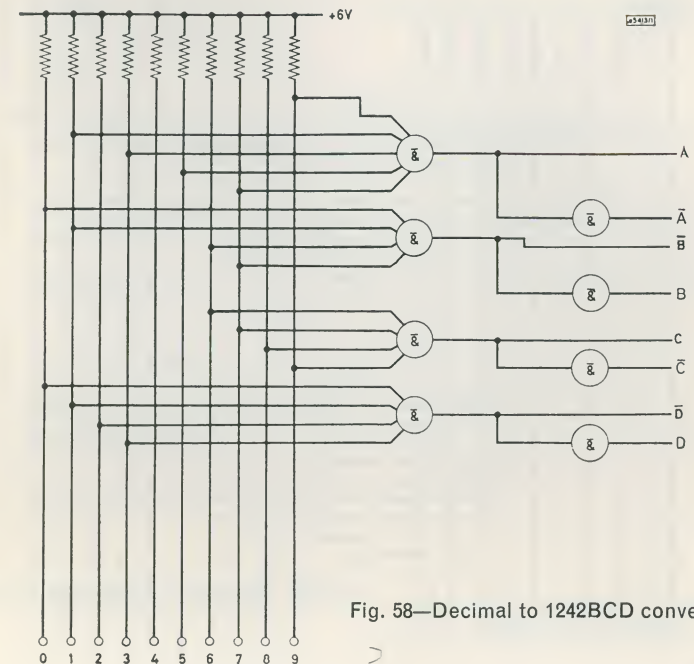


Fig. 58—Decimal to 1242BCD converter

Truth Table

	D Weight = 2	C 4	B 2	A 1
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	1	0	1	0
5	1	0	1	1
6	1	1	0	0
7	1	1	0	1
8	1	1	1	0
9	1	1	1	1

DECIMAL TO AIKEN CODE CONVERTER

All inputs are high except the energised number

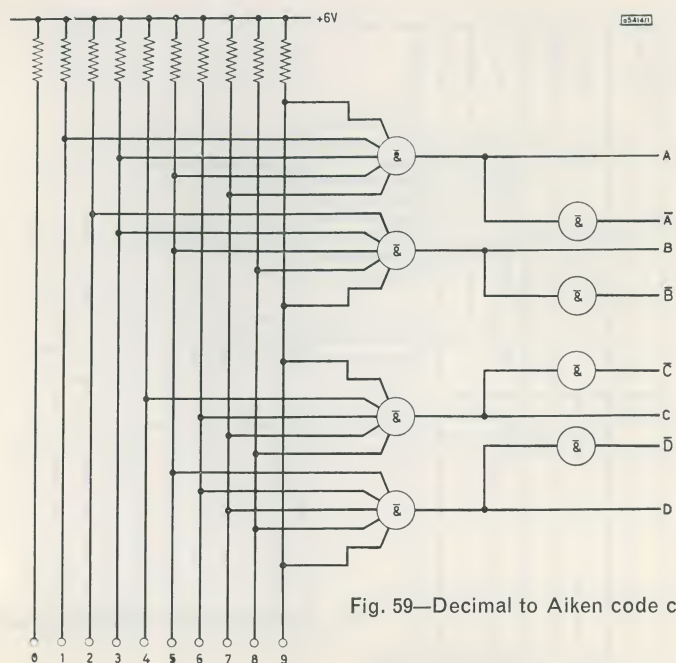


Fig. 59—Decimal to Aiken code converter

Truth Table				
	D Weight = 2	C 4	B 2	A 1
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	0	1
8	1	1	1	0
9	1	1	1	1

DECIMAL TO EXCESS-THREE CODE CONVERTER

All inputs are high except the energised number

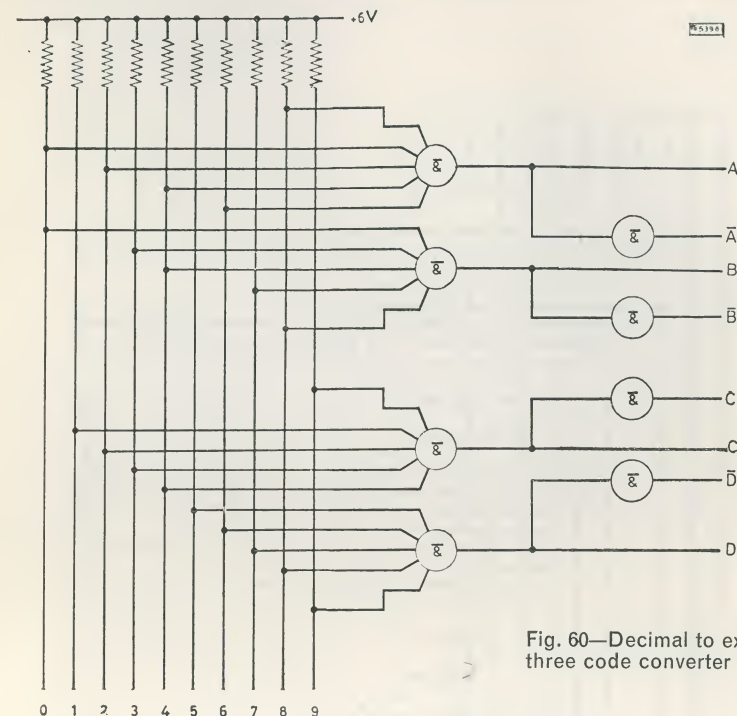


Fig. 60—Decimal to excess-three code converter

Truth Table				
	D	C	B	A
0	0	0	1	1
1	0	1	0	0
2	0	1	0	1
3	0	1	1	0
4	0	1	1	1
5	1	0	0	0
6	1	0	0	1
7	1	0	1	0
8	1	0	1	1
9	1	1	0	0

DECIMAL TO JOHNSON CODE CONVERTER

All inputs are high except the energised number

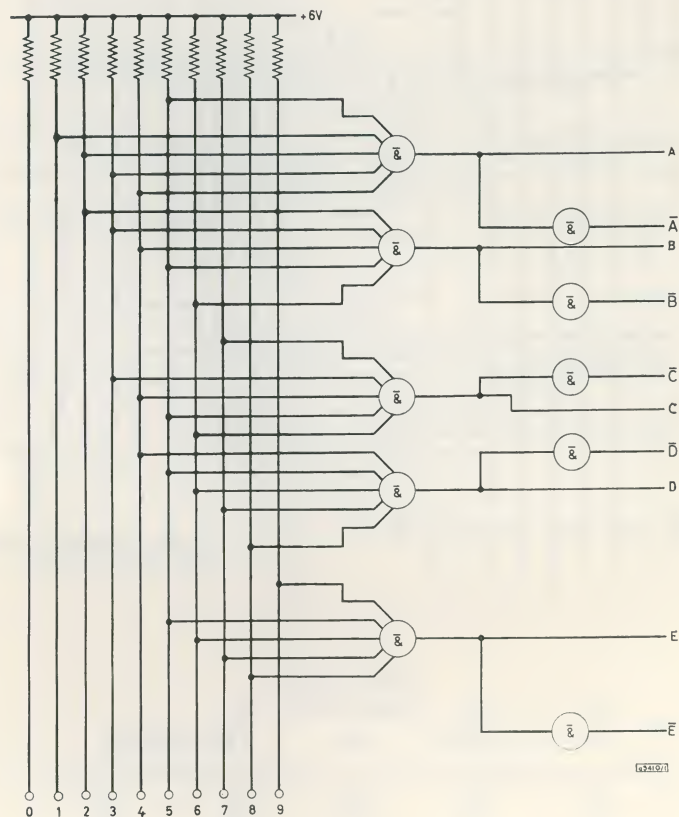


Fig. 61—Decimal to Johnson code converter

Truth Table

	E	D	C	B	A
0	0	0	0	0	0
1	0	0	0	0	1
2	0	0	0	1	1
3	0	0	1	1	1
4	0	1	1	1	1
5	1	1	1	1	1
6	1	1	1	1	0
7	1	1	1	0	0
8	1	1	0	0	0
9	1	0	0	0	0

JOHNSON CODE TO 1248BCD CONVERTER

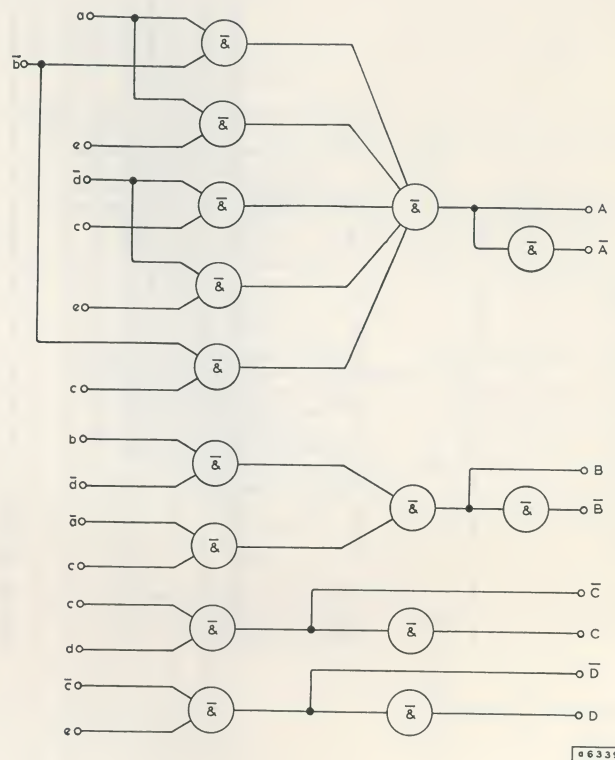


Fig. 62—Johnson code to 1248BCD converter

Truth Table

Johnson					1248BCD			
e	d	c	b	a	D	C	B	A
0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	1
0	0	0	1	1	0	0	1	0
0	0	1	1	1	0	0	1	1
0	1	1	1	1	0	1	0	0
1	1	1	1	1	0	1	0	1
1	1	1	1	0	0	1	1	0
1	1	1	0	0	0	1	1	1
1	1	0	0	0	1	0	0	0
1	0	0	0	0	1	0	0	1

GRAY CODE TO 1248BCD CONVERTER Gray code with a cycle length of 10

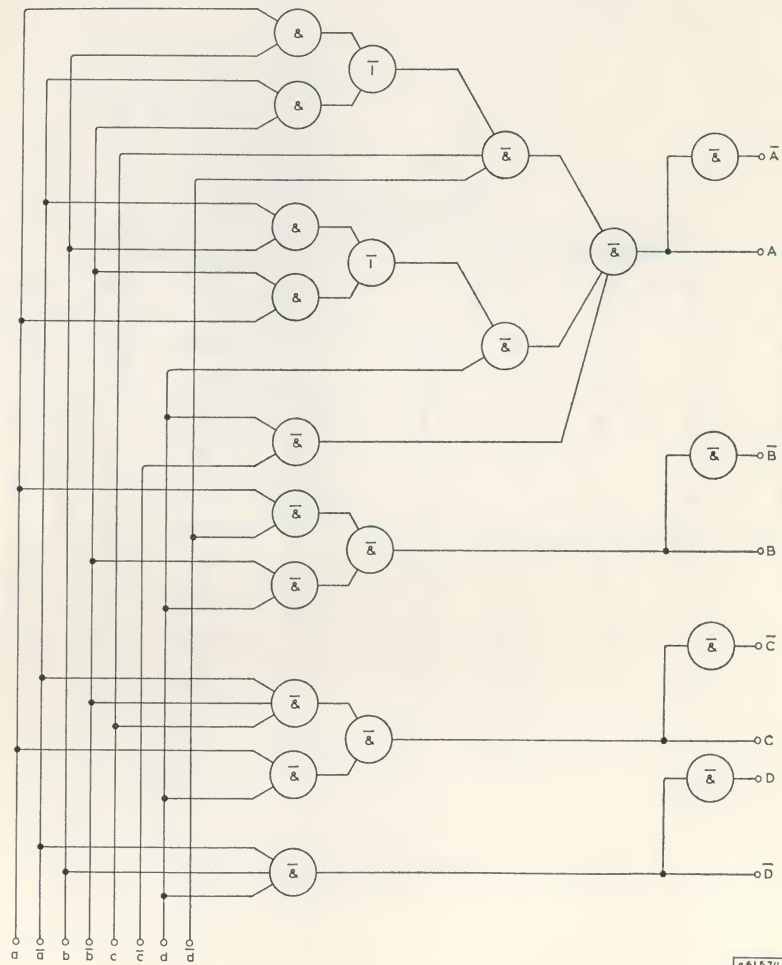


Fig. 63—Gray code to 1248BCD converter

Truth Table

d	Gray			1248BCD			
	c	b	a	D	C	B	A
0	0	1	0	0	0	0	0
0	1	1	0	0	0	0	1
0	1	1	1	0	0	1	0
0	1	0	1	0	0	1	1
0	1	0	0	0	1	0	0
1	1	0	0	0	1	0	1
1	1	0	1	0	1	1	0
1	1	1	1	0	1	1	1
1	1	1	0	1	0	0	0
1	0	1	0	1	0	0	1

GRAY CODE TO BINARY CONVERTER

Gray code with a cycle length of 16

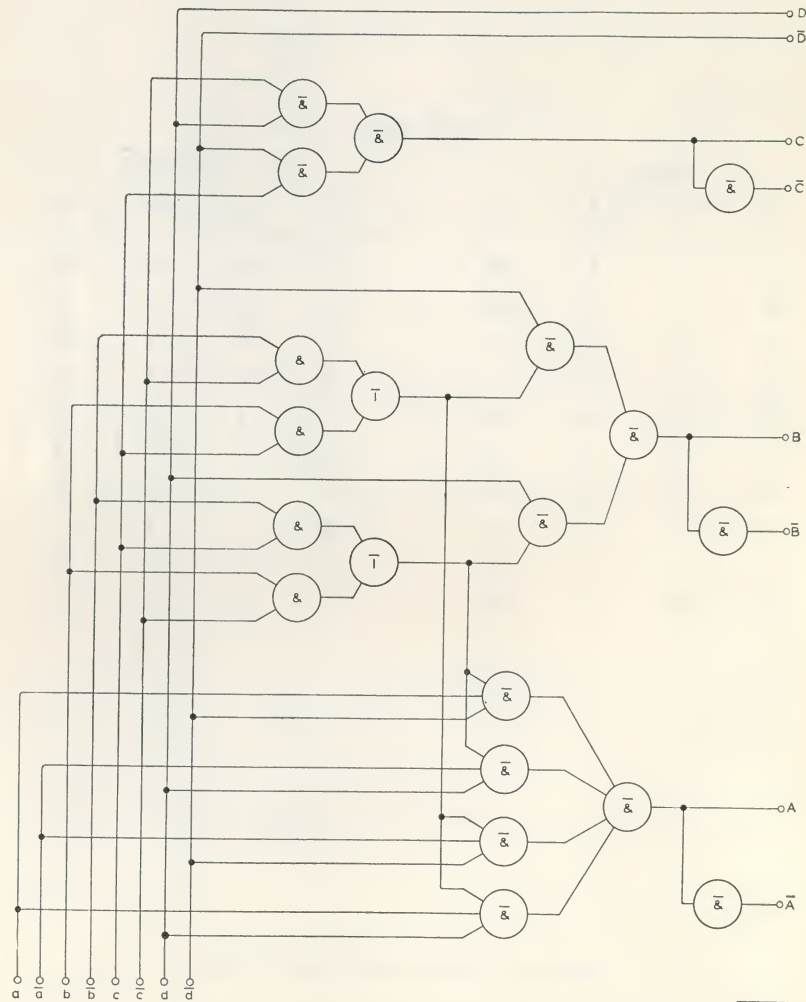


Fig. 64—Gray code to binary converter

Truth Table

Gray				Binary			
d	c	b	a	D	C	B	A
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	1	0	0	1	0
0	0	1	0	0	0	1	1
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	1
0	1	0	1	0	1	1	0
0	1	0	0	0	1	1	1
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	1
1	1	1	1	1	0	1	0
1	1	1	0	1	0	1	1
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	0	0	1	1	1	1	0
1	0	0	0	1	1	1	1

CHAPTER 7

ERROR DETECTORS

Errors can be detected either by recognising redundant states and giving a signal if one occurs or by means of a "parity check". In this chapter, three circuits of the "redundant state detector" type and one of the "parity check" type are given.

A parity check is effected by generating a signal—the parity signal—which is either a '1' or a '0' depending on whether the number of '1' bits in the relevant row of the truth table is even or odd respectively. The sum of the '1' bits in a number, together with its parity signal should, therefore, always be an odd number. An error becomes evident if the number, together with its parity bit, is found to contain an even number of '1' bits.

1248BCD ERROR DETECTOR

 


Fig. 65—1248BCD error detector circuit

	Truth Table			
	D	C	B	A
Weight = 8	4	2	1	
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
Redundant	1	0	1	0
	1	0	1	1
	1	1	0	0
	1	1	0	1
	1	1	1	0
	1	1	1	1

The Boolean expression for the presence of a redundant state is:
 $\bar{A}.B.\bar{C}.D + A.B.\bar{C}.D + \bar{A}.B.C.D + A.B.C.D + \bar{A}.B.C.D + A.B.C.D$,
 which can be simplified to

$$D(B+C).$$

EXCESS-THREE CODE ERROR DETECTOR

 


Fig. 66—Excess-three code error detector

	Truth Table			
	D	C	B	A
Redundant	0	0	0	0
	0	0	0	1
	0	0	1	0
0	0	0	1	1
1	0	1	0	0
2	0	1	0	1
3	0	1	1	0
4	0	1	1	1
5	1	0	0	0
6	1	0	0	1
7	1	0	1	0
8	1	0	1	1
9	1	1	0	0
Redundant	1	1	0	1
	1	1	1	0
	1	1	1	1

The Boolean expression for the presence of a redundant state is:
 $\bar{A}.B.\bar{C}.D + A.B.\bar{C}.D + \bar{A}.B.C.D + A.B.C.D + \bar{A}.B.C.D + A.B.C.D$,
 which can be simplified to:

$$\bar{B}.\bar{C}.D + B.C.D + A.C.D + \bar{A}.\bar{C}.\bar{D}.$$

AIKEN CODE ERROR DETECTOR

 


Fig. 67—Aiken code error detector

56338

Truth Table

	D Weight = 2	C 4	B 2	A 1
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	0	1
8	1	1	1	0
9	1	1	1	1

The following states are redundant

0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0

The Boolean expression for the presence of a redundant state is:

$A.\bar{B}.C.\bar{D} + \bar{A}.B.C.\bar{D} + A.B.C.\bar{D} + \bar{A}.\bar{B}.\bar{C}.D + A.\bar{B}.\bar{C}.D + \bar{A}.B.\bar{C}.D$,
which can be simplified to:

$$A.C.\bar{D} + \bar{A}.\bar{C}.D + B.C.\bar{D} + \bar{B}.\bar{C}.D.$$

PARITY CHECKER

The parity checker shown in Fig. 68 operates in the serial mode.

Initially the J-K bistable circuit is set to '0'. Information from the sending register is then transferred to the series of D bistable elements which form a shift register. The reset terminal of the J-K bistable element is released, and the contents of the shift register are fed serially, via routing circuits, to the receiving register. Each time a '1' appears in the final stage of the shift register, the J-K bistable element changes state. The final state of the J-K bistable element is, therefore, determined by whether the number of '1' bits is odd or even.

The shift register is controlled by a pulse generator which is inhibited when the content of the shift register is 000.

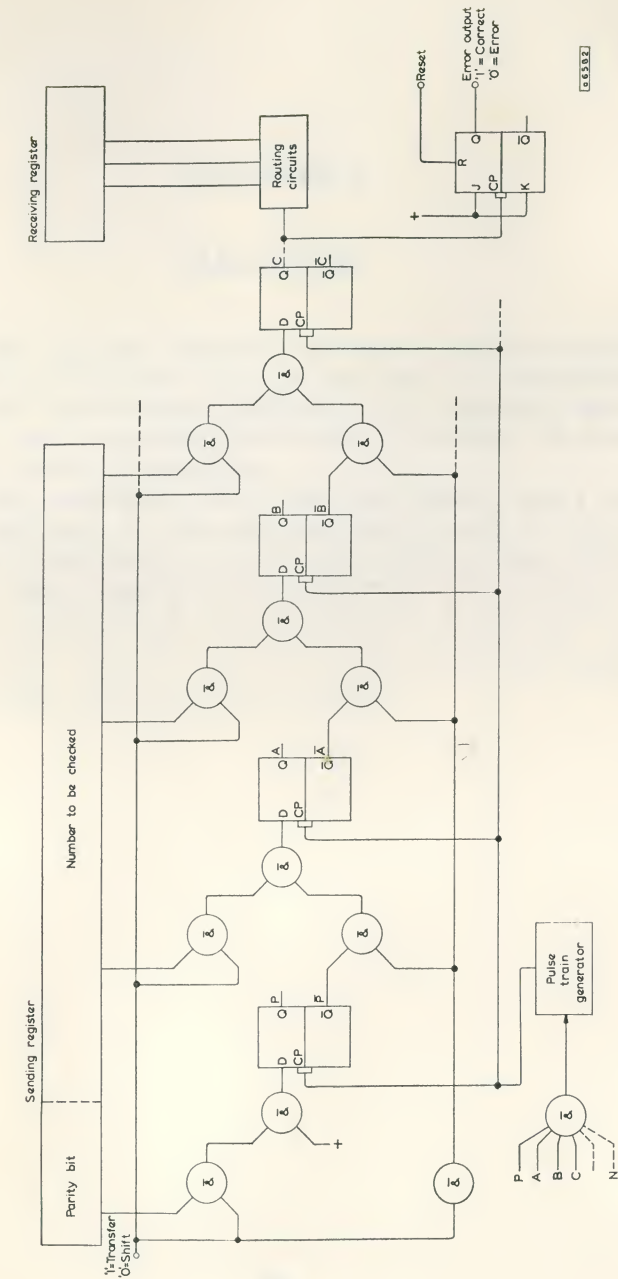


Fig. 68—Parity checker for N bits

CHAPTER 8

ADDERS

The four most important arithmetic operations—addition, subtraction, multiplication and division—can all be performed by manipulations of addition, and, for this reason, addition is a very important operation. The circuits used to perform the function of addition fall into two groups—half adders and full adders.

A half adder produces the sum of two bits, together with a carry if necessary. Each stage of a full adder can handle one bit of each of the numbers to be added and the carry from the previous stage. Adders can operate in a serial or parallel mode. In the serial mode, addition occurs sequentially, starting with the least significant bit. In the parallel mode, addition of all the bits is effected simultaneously. Parallel adders perform the total addition operation much more quickly than serial adders but are more complex and therefore more expensive.

HALF ADDERS

 


Fig. 69—Half adder using one FJH131

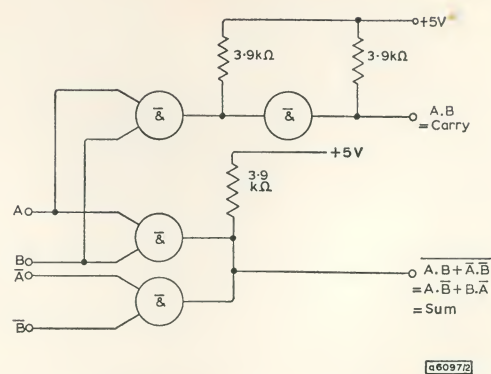


Fig. 70—Half adder using one FJH231

 


Fig. 71—Half adder using AND-OR-NOT and NAND gates

 


Fig. 72—Half adder using NAND gates

Truth Table			
Inputs		Outputs	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

The Boolean expressions for the sum and carry are:

$$S = A \cdot \bar{B} + B \cdot \bar{A}, \quad C = A \cdot B.$$

FULL ADDERS

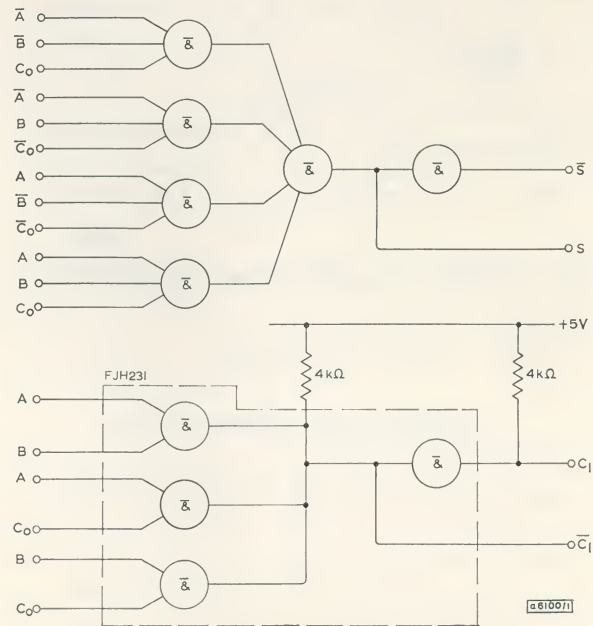


Fig. 73—Full adder using NAND gates

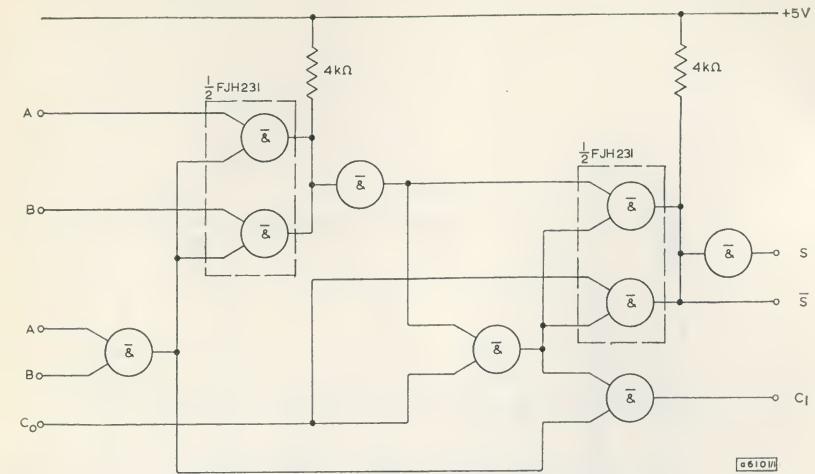


Fig. 74—Full adder using NAND gates

Truth Table				
Inputs			Outputs	
C ₀	A	B	S	C ₁
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	1	0	0	1
1	0	1	0	1
1	1	1	1	1

The Boolean expressions for the sum and carry are:

$$S_1 = \bar{A} \cdot \bar{B} \cdot C_0 + \bar{A} \cdot B \cdot \bar{C}_0 + A \cdot \bar{B} \cdot \bar{C}_0 + A \cdot B \cdot C_0$$

$$C_1 = A \cdot B + A \cdot C_0 + B \cdot C_0$$

FOUR-BIT BINARY ADDER

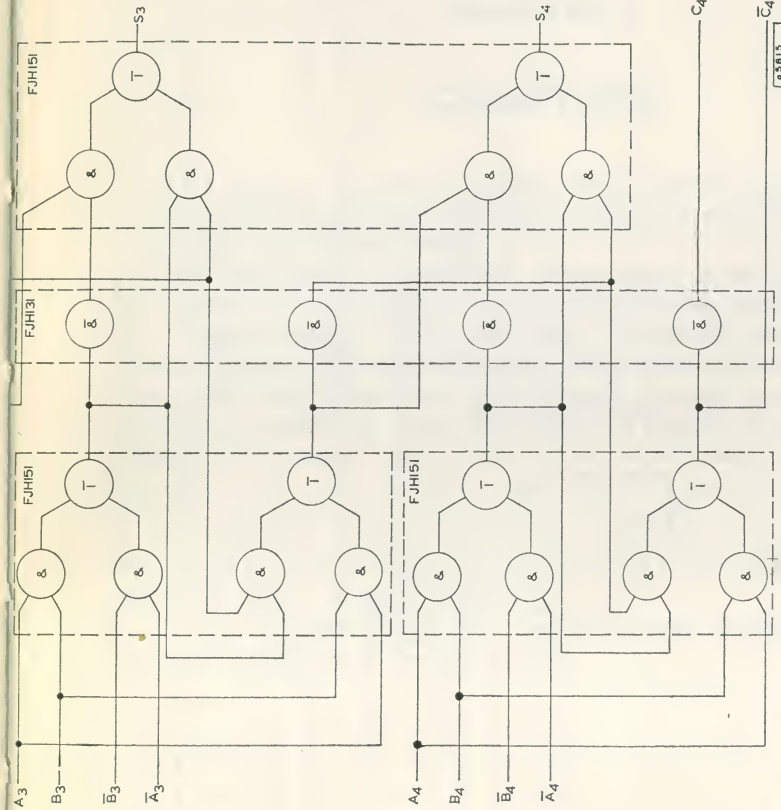
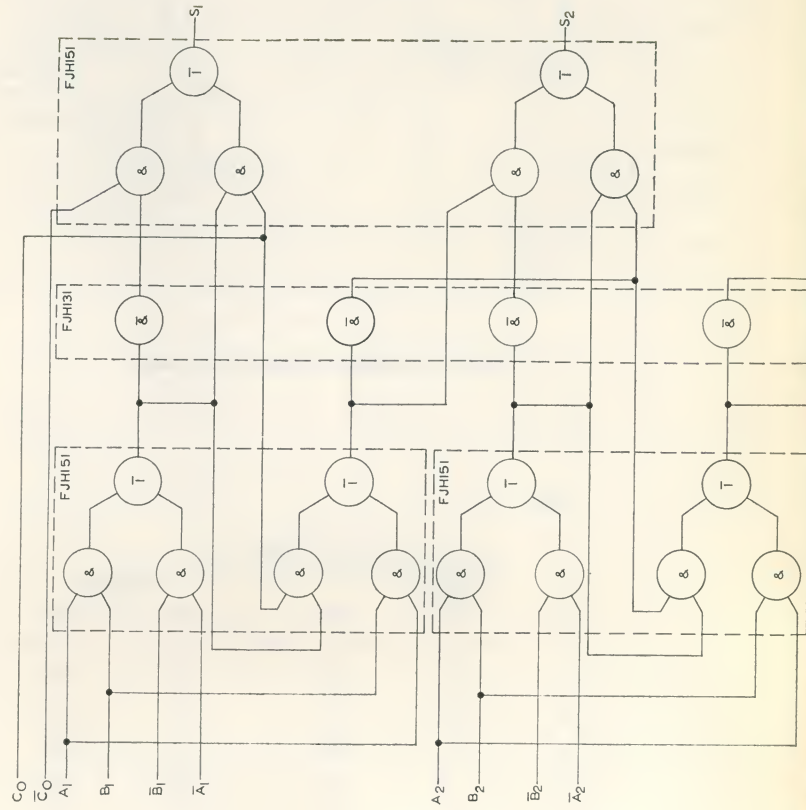


Fig. 75—Four-bit binary adder

SERIAL ADDER

The carry signal is stored in the D bistable element. The input to shift registers A and B may be serial or parallel.

Three shift registers are shown although the sum could be stored in one of the input shift registers.

The carry signal is stored in the D bistable element. The input to shift registers A and B may be serial or parallel.

Three shift registers are shown although the sum could be stored in one of the input shift registers.

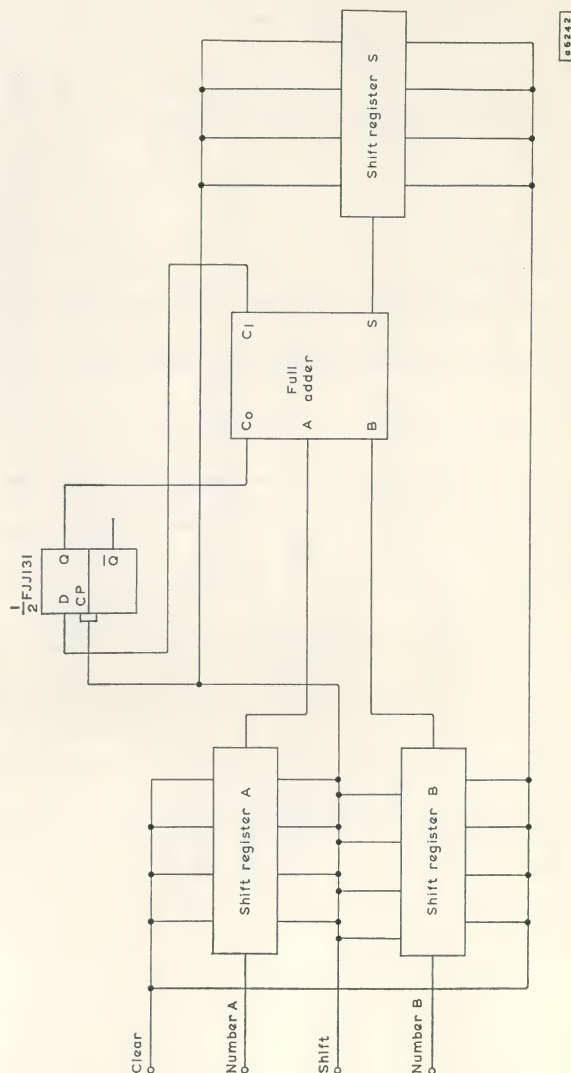


Fig. 76—Block diagram of serial adder

CHAPTER 9

The FJ range of integrated bistable circuits can be used to make synchronous or asynchronous counters operating in any desired code and counting to any desired number.

In an asynchronous counter, the trigger input of each bistable circuit is connected to the output of the preceding bistable circuit. This results in a "ripple-through" of the count pulses, so that the last bistable circuit cannot change its state until all the preceding bistable circuits have changed state. The delay inherent in ripple-through counters is avoided in synchronous counters by using the outputs of bistable circuits as gating signals to the count pulses which are fed to all bistable circuits in the counter. In this way, all those stages that are required to change state when a particular count pulse arrives will change simultaneously.

The differences between synchronous and asynchronous counters are illustrated in Figs. 77 and 79, which show an asynchronous and a synchronous binary counter respectively.

The use of multiple-input J-K bistable elements simplifies gating and reduces the number of devices required.

ASYNCHRONOUS BINARY UP COUNTER

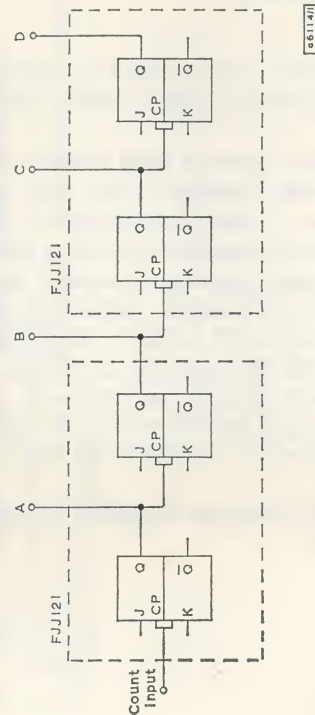


Fig. 77—Asynchronous binary up counter

 


Fig. 78—Waveforms for asynchronous binary up counter

Truth Table

	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1

SYNCHRONOUS BINARY UP COUNTER

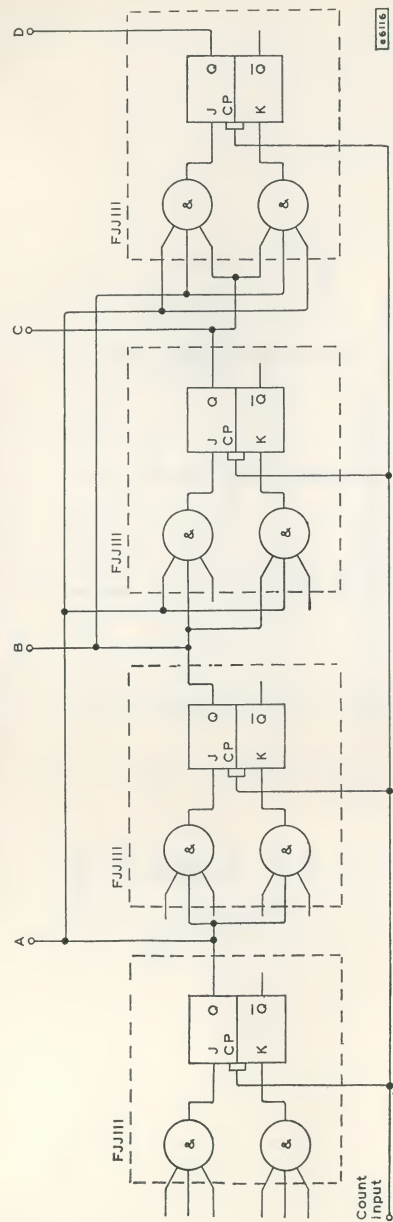


Fig. 79—Synchronous binary up counter

 


Fig. 80—Waveforms for synchronous binary up counter

Truth Table

	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1

ASYNCHRONOUS BINARY DOWN COUNTER

 


Fig. 81—Asynchronous binary down counter

Truth Table

	D	C	B	A
0	0	0	0	0
15	1	1	1	1
14	1	1	1	0
13	1	1	0	1
12	1	1	0	0
11	1	0	1	1
10	1	0	1	0
9	1	0	0	1
8	1	0	0	0
7	0	1	1	1
6	0	1	1	0
5	0	1	0	1
4	0	1	0	0
3	0	0	1	1
2	0	0	1	0
1	0	0	0	1

SYNCHRONOUS BINARY DOWN COUNTER

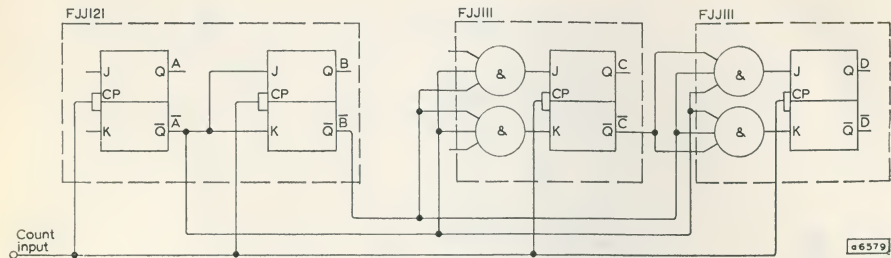


Fig. 82—Synchronous binary down counter

Truth Table

	D	C	B	A
0	0	0	0	0
15	1	1	1	1
14	1	1	1	0
13	1	1	0	1
12	1	1	0	0
11	1	0	1	1
10	1	0	1	0
9	1	0	0	1
8	1	0	0	0
7	0	1	1	1
6	0	1	1	0
5	0	1	0	1
4	0	1	0	0
3	0	0	1	1
2	0	0	1	0
1	0	0	0	1

REVERSIBLE SYNCHRONOUS BINARY COUNTER


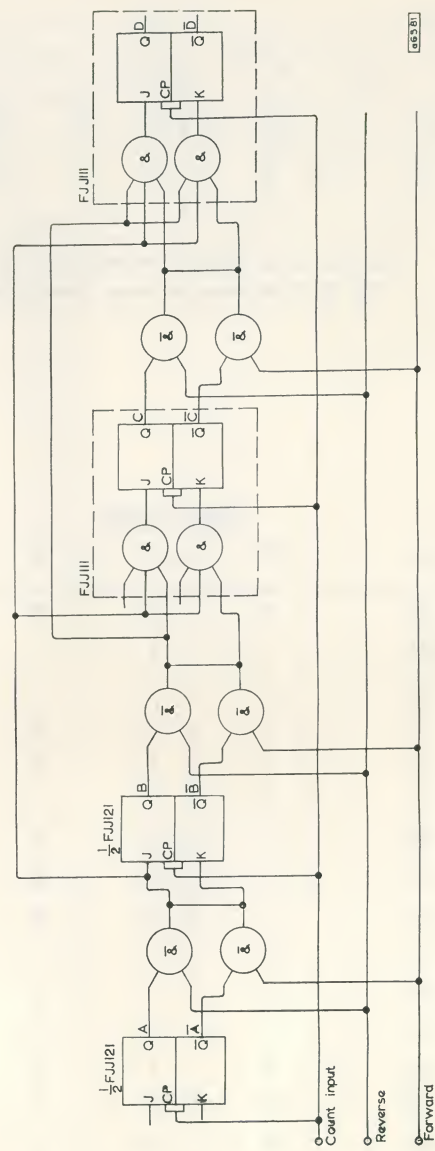


Fig. 83—Reversible synchronous binary counter

	Truth Table			
	D	C	B	A
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1

SYNCHRONOUS MODULO-3 UP COUNTER

 

Truth Table

	B	A
0	0	0
1	0	1
2	1	0

Fig. 84—Synchronous modulo-3 up counter

SYNCHRONOUS UNWEIGHTED MODULO-5 UP COUNTER

 


Fig 85—Synchronous unweighted modulo-5 counter

Truth Table

	C	B	A
0	0	0	0
1	0	0	1
2	0	1	1
3	1	1	0
4	1	0	0

SYNCHRONOUS MODULO-5 UP COUNTER

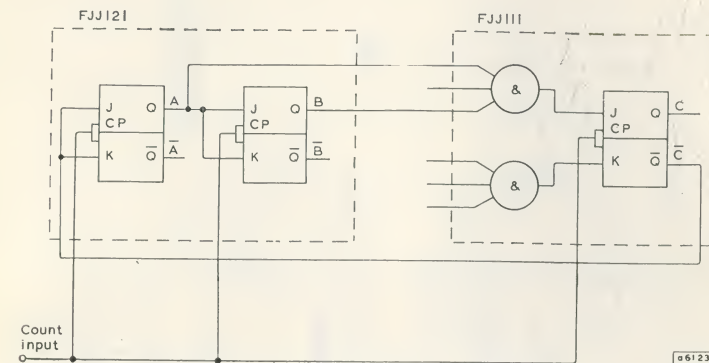


Fig. 86—Synchronous modulo-5 up counter

Truth Table

	C	B	A
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0

SYNCHRONOUS MODULO-6 UP COUNTER

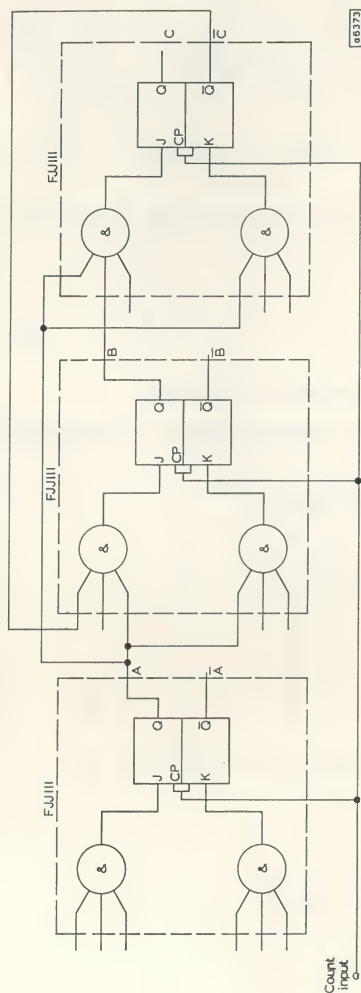



Fig. 87—Synchronous modulo-6 up counter

Truth Table

C	B	A
0	0	0
1	0	1
2	0	0
3	0	1
4	1	0
5	1	0

ASYNCHRONOUS 1248BCD UP COUNTER

Operating frequency $\geq 10\text{MHz}$

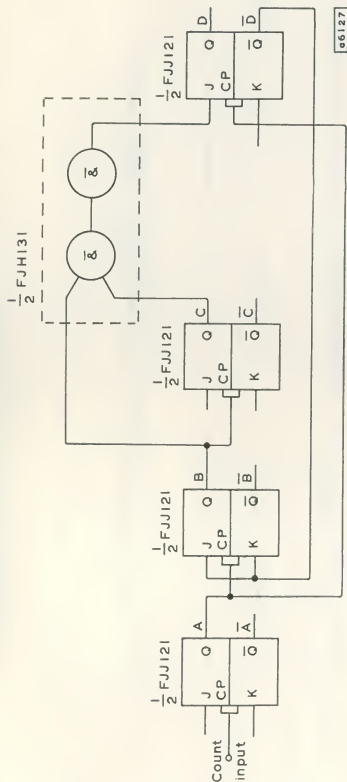

Truth Table

D	C	B	A
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0
9	0	0	1

Fig. 88—Asynchronous 1248BCD up counter

SYNCHRONOUS 1248BCD UP COUNTERS

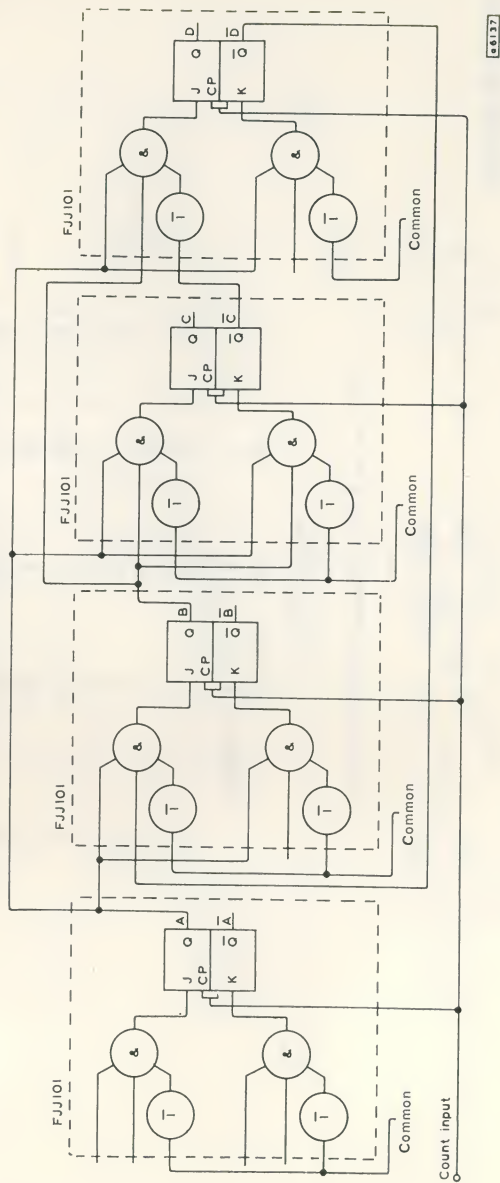


Fig. 89—Synchronous 1248BCD up counter using FJJ101 elements

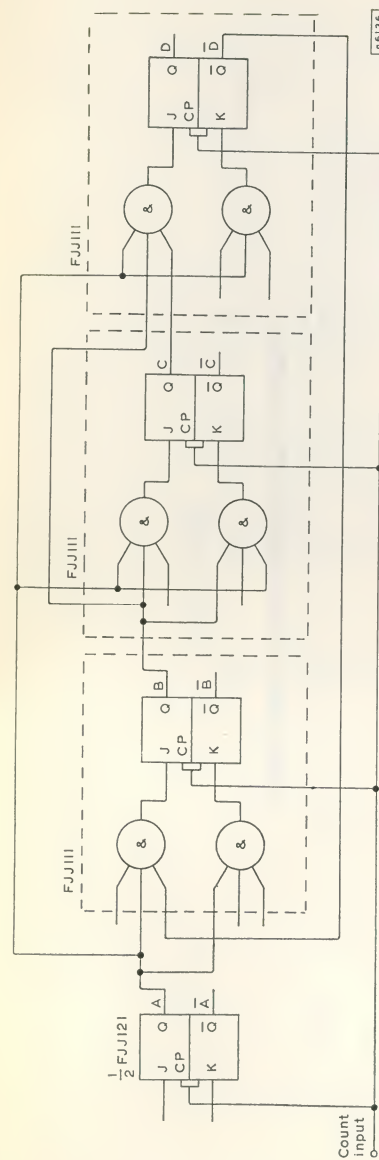


Fig. 90—Synchronous 1248BCD up counter using FJJ111 and FJJ121 elements

Truth Table

	D	C	B	A
Weight = 8	4	2	1	
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

ASYNCHRONOUS 1248BCD DOWN COUNTER

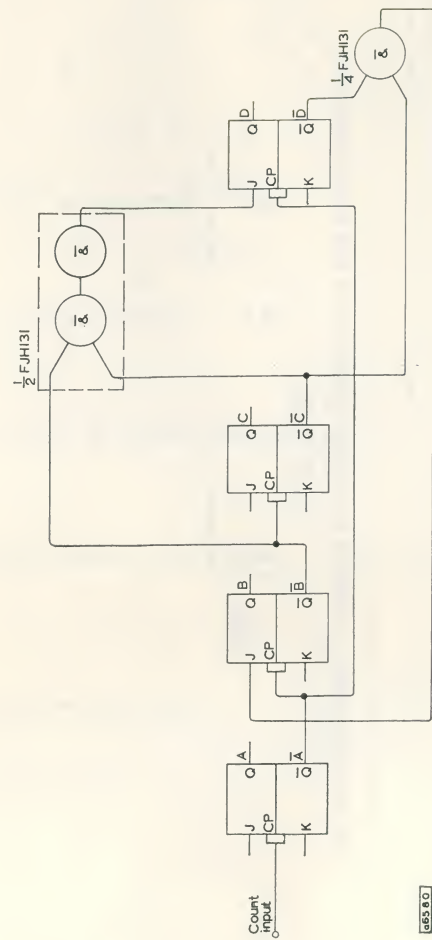


Fig. 91—Asynchronous 1248BCD down counter

SYNCHRONOUS 1248BCD DOWN COUNTER

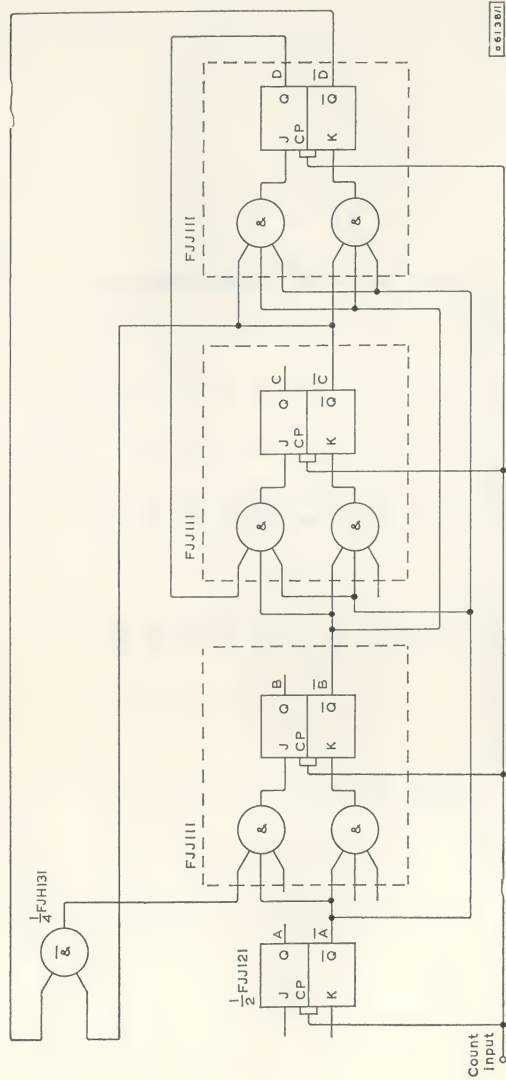


Fig. 92—Synchronous 1248BCD down counter

Truth Table

	D	C	B	A
Weight = 8	4	2	1	
0	0	0	0	0
9	1	0	0	1
8	1	0	0	0
7	0	1	1	1
6	0	1	1	0
5	0	1	0	1
4	0	1	0	0
3	0	0	1	1
2	0	0	1	0
1	0	0	0	1

SYNCHRONOUS REVERSIBLE 1248BCD COUNTER

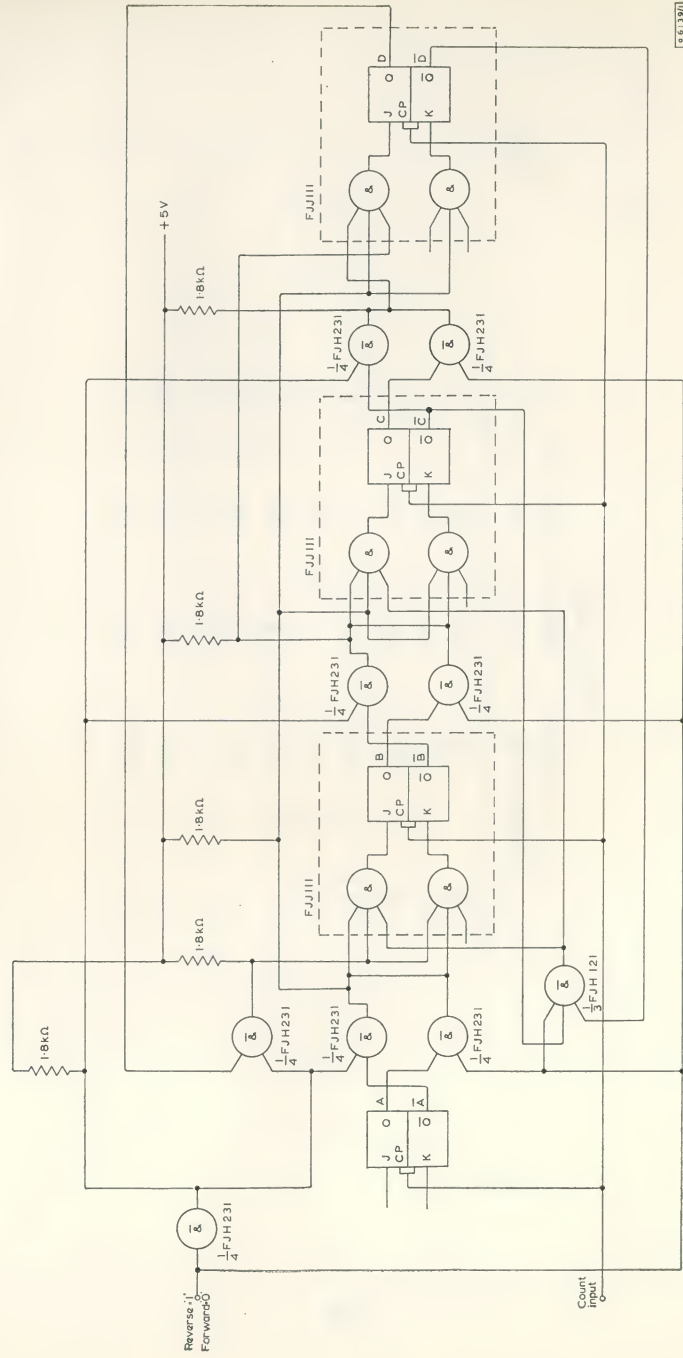


Fig. 93—Reversible 1248BCD counter using multiple-input J-K bistable elements and NAND gates

Truth Table

Weight = 8				D	C	B	A
0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	1
2	0	0	0	0	0	1	0
3	0	0	0	0	0	1	1
4	0	0	1	0	1	0	0
5	0	0	1	0	1	0	1
6	0	0	1	1	0	0	0
7	0	0	1	1	0	0	1
8	1	0	0	0	0	0	0
9	1	0	0	0	0	0	1

SYNCHRONOUS REVERSIBLE 1248BCD COUNTER


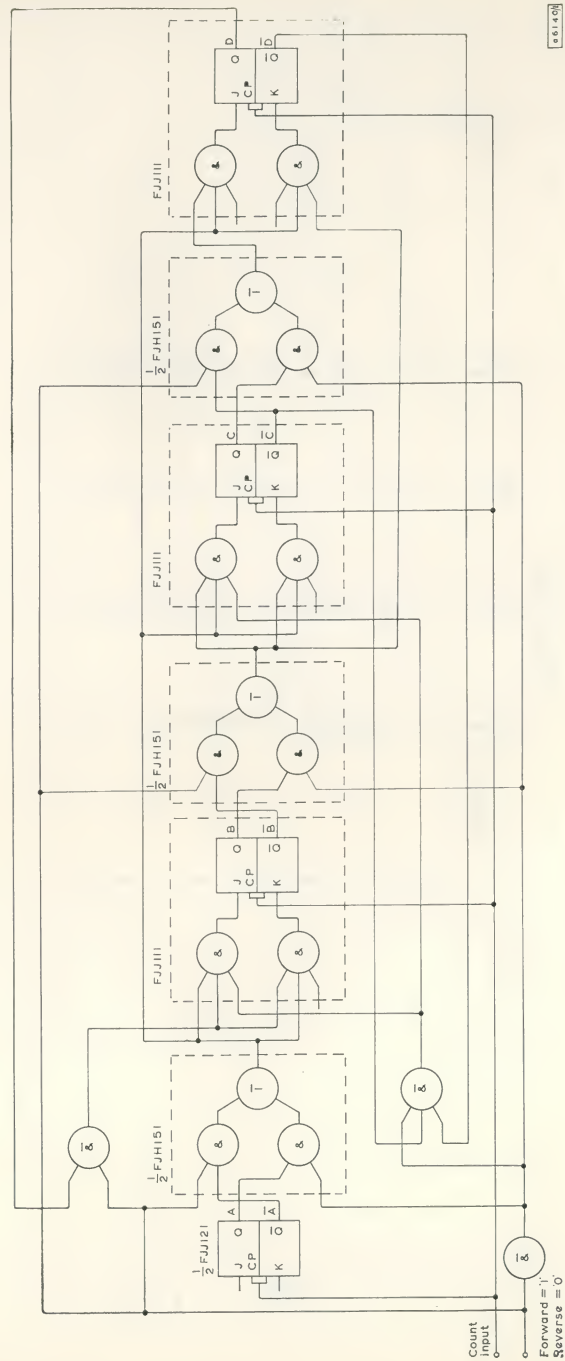


Fig. 94—Reversible 1248BCD counter using multiple-input J-K bistable elements, NAND gates and AND-OR-NOT gates

Truth Table

	D	C	B	A
Weight = 8	4	2	1	
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

SYNCHRONOUS EXCESS-THREE CODE UP COUNTER

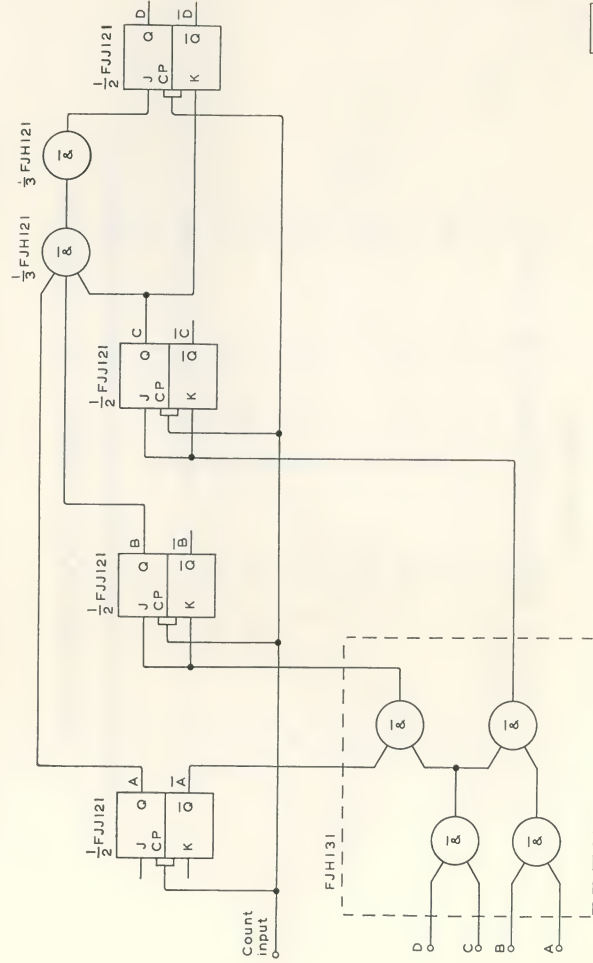

66144

Fig. 96--Excess-three code up counter

Truth Table

	D	C	B	A
0	0	0	1	1
1	0	1	0	0
2	0	1	0	1
3	0	1	1	0
4	0	1	1	1
5	1	0	0	0
6	1	0	0	1
7	1	0	1	0
8	1	0	1	1
9	1	1	0	0

SYNCHRONOUS AIKEN CODE UP COUNTER

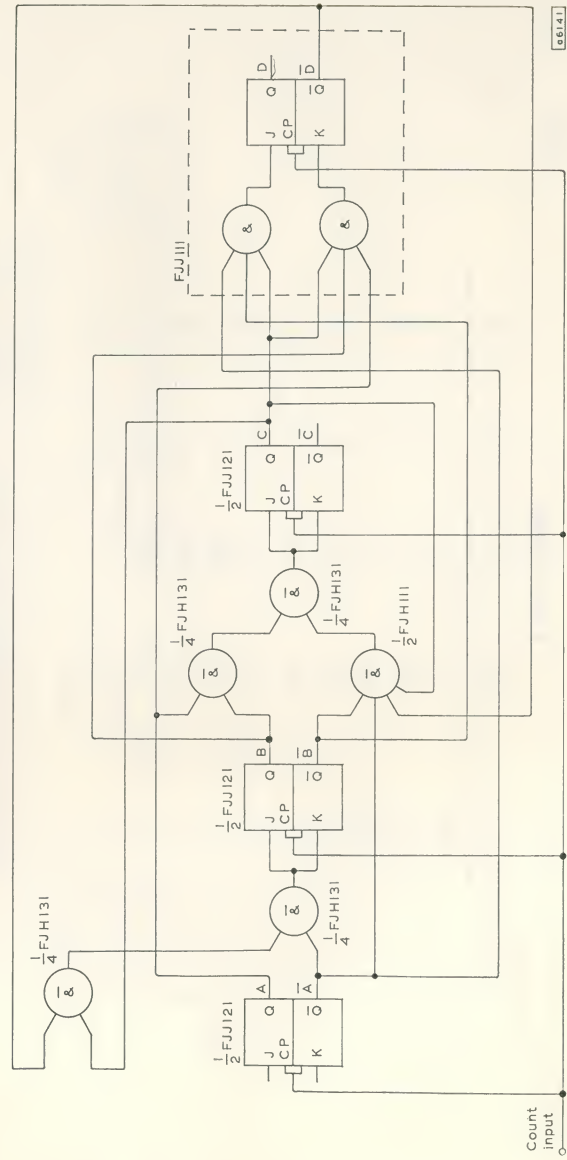


Fig. 97—Synchronous Aiken code up counter

Truth Table

	D	C	B	A
Weight = 2	4	2	1	
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	0	1
8	1	1	1	0
9	1	1	1	1

TWISTED-RING, OR JOHNSON, COUNTER

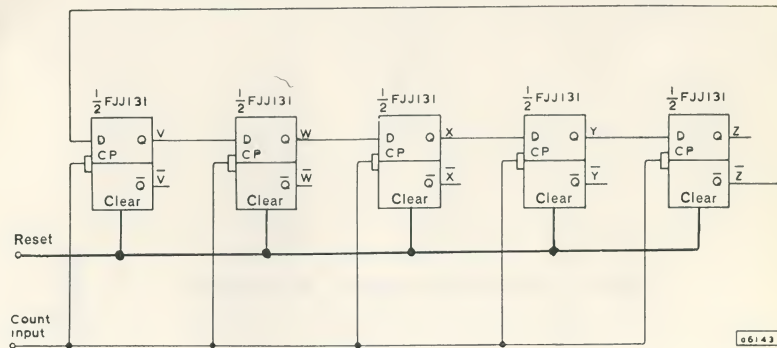


Fig. 98—Twisted-ring, or Johnson, counter

Truth Table					
	Z	Y	X	W	V
0	0	0	0	0	0
1	0	0	0	0	1
2	0	0	0	1	1
3	0	0	1	1	1
4	0	1	1	1	1
5	1	1	1	1	1
6	1	1	1	1	0
7	1	1	1	0	0
8	1	1	0	0	0
9	1	0	0	0	0

SYNCHRONOUS 1248 WEIGHTED UP COUNTER WITH A CYCLE LENGTH OF TWELVE

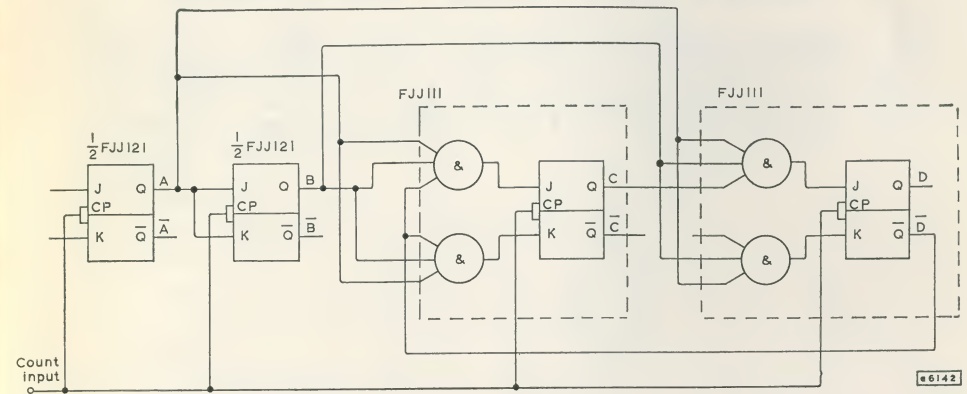


Fig. 99—Synchronous 1248 weighted counter with a cycle length of twelve

Truth Table				
	D Weight = 8	C 4	B 2	A 1
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1

CHAPTER 10

COUNTERS USING THE FJJ141

The FJJ141 consists of four master-slave J-K bistable elements with internal gating which enables a count of ten to be obtained in two ways. Alternatively, counts of 2 and 5 may be obtained independently. While counting is in progress, pins 2 or 3 and 6 or 7 must be connected to the "common" line.

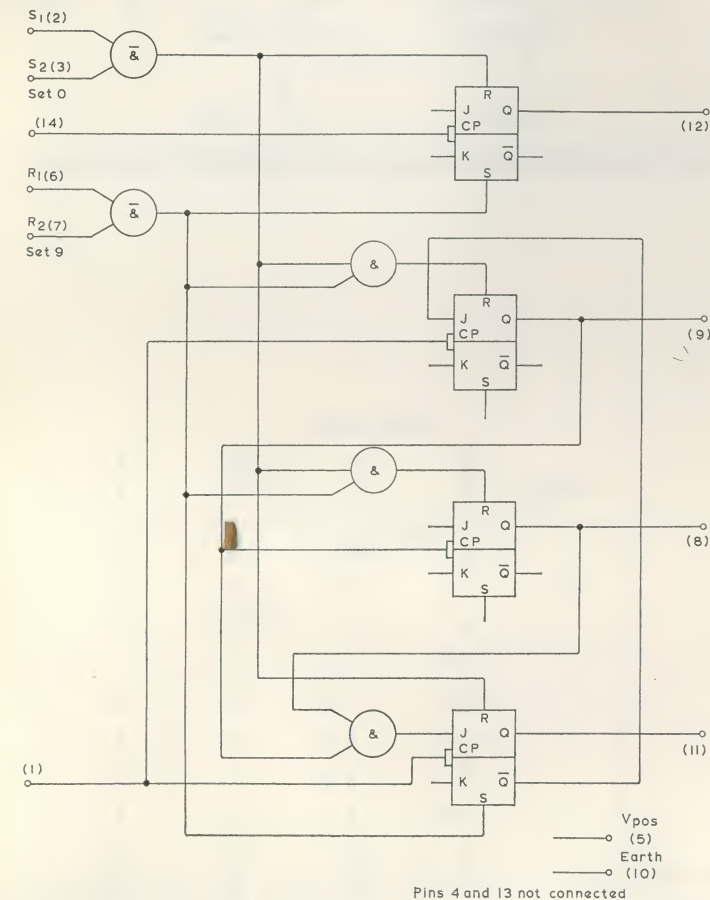


Fig. 100—Block diagram of FJJ141 element. The figures in brackets refer to the pin numbers

1248BCD DECADE COUNTER

 


Fig. 101—The FJJ141 element connected as a 1248BCD decade counter

Truth Table				
	D Weight = 8	C 4	B 2	A 1
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

To set to zero, pin 2 or 3 (or both) and pin 6 or 7 (or both) must be connected to the "common" line.

MODULO-5 COUNTER

 


Fig. 102—The FJJ141 element used as a modulo-5 counter

Truth Table			
	D Weight = 4	C 2	B 1
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0

To set to zero, pin 2 or 3 (or both) and pin 6 or 7 (or both) must be connected to the "common" line.

Bistable element A may be used independently. The input to bistable element A is pin 14 and the output pin 12.

1245BCD COUNTER

This is a divide-by-ten counter which gives a mark:space ratio of 1:1 on pin 12.

 


Fig. 103—The FJJ141 connected as a divide-by-ten counter counting in 1245BCD

Truth Table				
	D	C	B	A
Weight = 5	4	2	1	
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	1	0	0	0
6	1	0	0	1
7	1	0	1	0
8	1	0	1	1
9	1	1	0	0

To set to zero, pin 2 or 3 (or both) and pin 6 or 7 (or both) must be connected to the positive line.

CHAPTER 11

CHAIN CODE GENERATORS

Chain code generators, sometimes referred to as pseudo-random generators, are used to provide division by some whole number, where the code used is of no importance. These circuits can frequently result in economies over conventional counters. Chain code generators are made by applying feedback to a shift register and feeding a '0' or a '1' into the shift register, depending upon its current contents. The maximal code generators give a cycle length of $2^n - 1$ states, where n is the number of stages. Generators which do not generate the maximal code—that is, with cycle lengths of less than $2^n - 1$ —can easily be made by applying different feedbacks to the shift register. One example of this is the Johnson counter. In the event of each stage being in the '0' state when the counter is switched on, a gate is inserted to detect this condition and to set up the correct initial state.

An alternative method of generating a shorter cycle length is to detect one state, by means of a gate, and use the output of the gate to set a different state in the chain code generator. This causes part of the normal sequence to be omitted, and thereby shortens the cycle length.

THREE-STAGE CHAIN CODE GENERATORS WITH CYCLE LENGTHS OF SEVEN

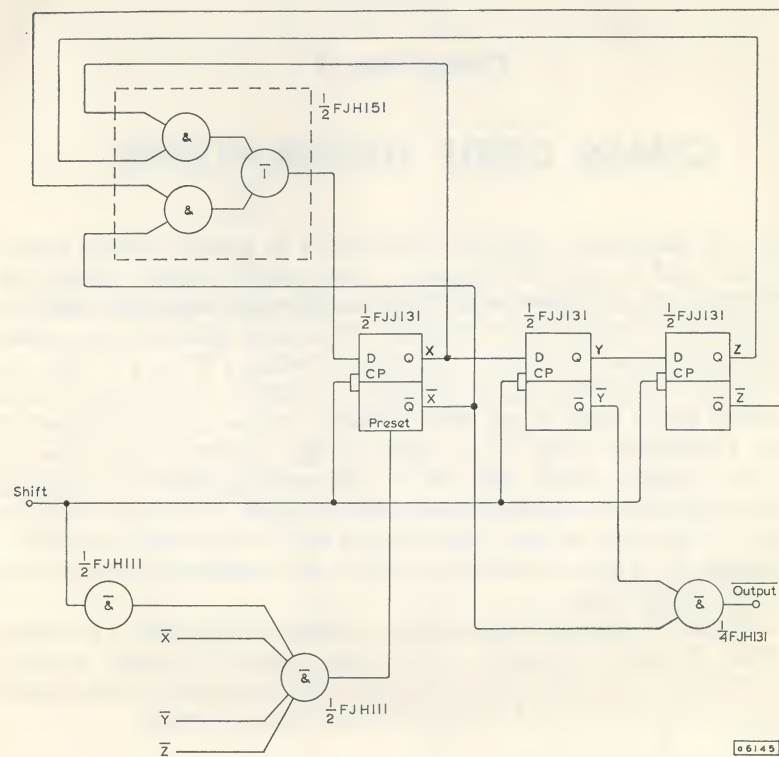


Fig. 104—Three-stage chain code generator with cycle length of seven

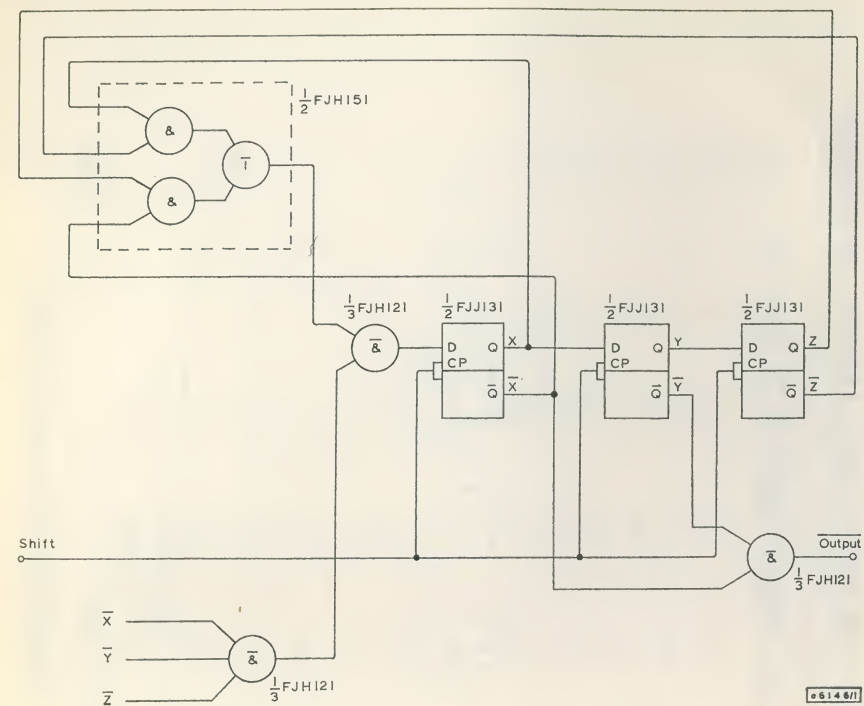


Fig. 105—Alternative three-stage chain code generator with cycle length of seven

Truth Table			
Z	Y	X	F
0	0	1	1
0	1	1	1
1	1	1	0
1	1	0	1
1	0	1	0
0	1	0	0
1	0	0	1

The Boolean expression for the feedback factor, F, is given by $F = \bar{X}.Z + X.\bar{Z}$.

FOUR-STAGE CHAIN CODE GENERATOR WITH CYCLE LENGTH OF FIFTEEN

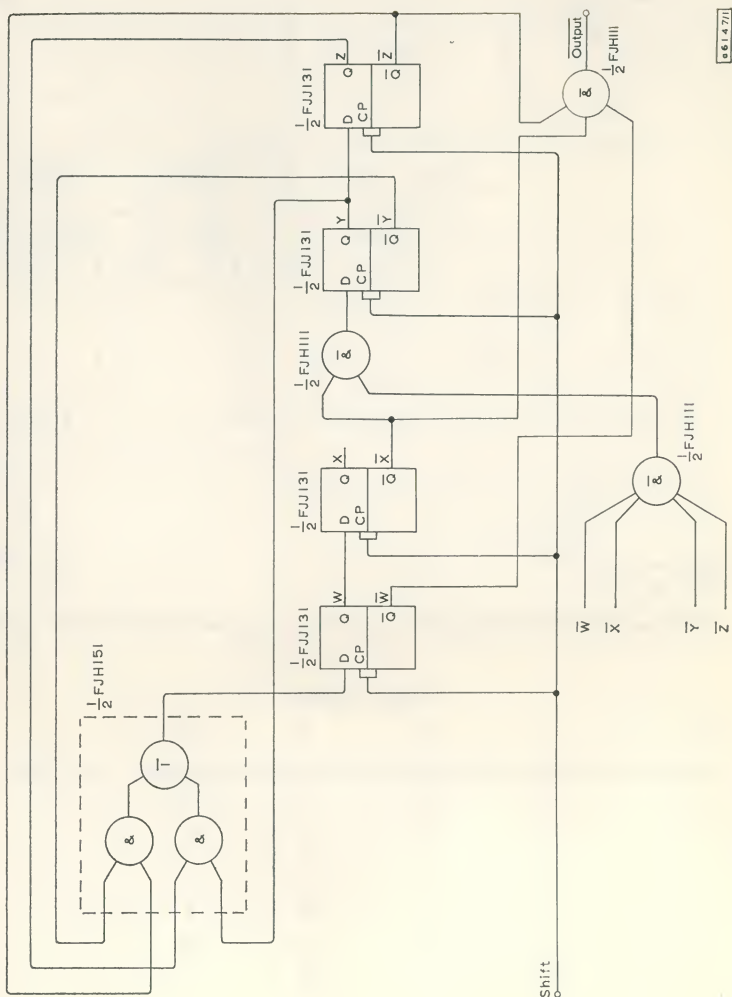


Fig. 106—Four-stage chain code generator with cycle length of fifteen

Truth Table

Z	Y	X	W	F
0	1	0	0	1
1	0	0	1	1
0	0	1	1	0
0	1	1	0	1
1	1	0	1	0
1	0	1	0	1
0	1	0	1	1
1	0	1	1	1
0	1	1	1	1
1	1	1	1	0
1	1	1	0	0
1	1	0	0	0
1	0	0	0	1
0	0	0	1	0
0	0	1	0	0

The Boolean expression for the feedback factor, F, is given by $F = Y \cdot \bar{Z} + \bar{Y} \cdot Z$.

ALTERNATIVE FOUR-STAGE GENERATOR WITH CYCLE LENGTH OF FIFTEEN

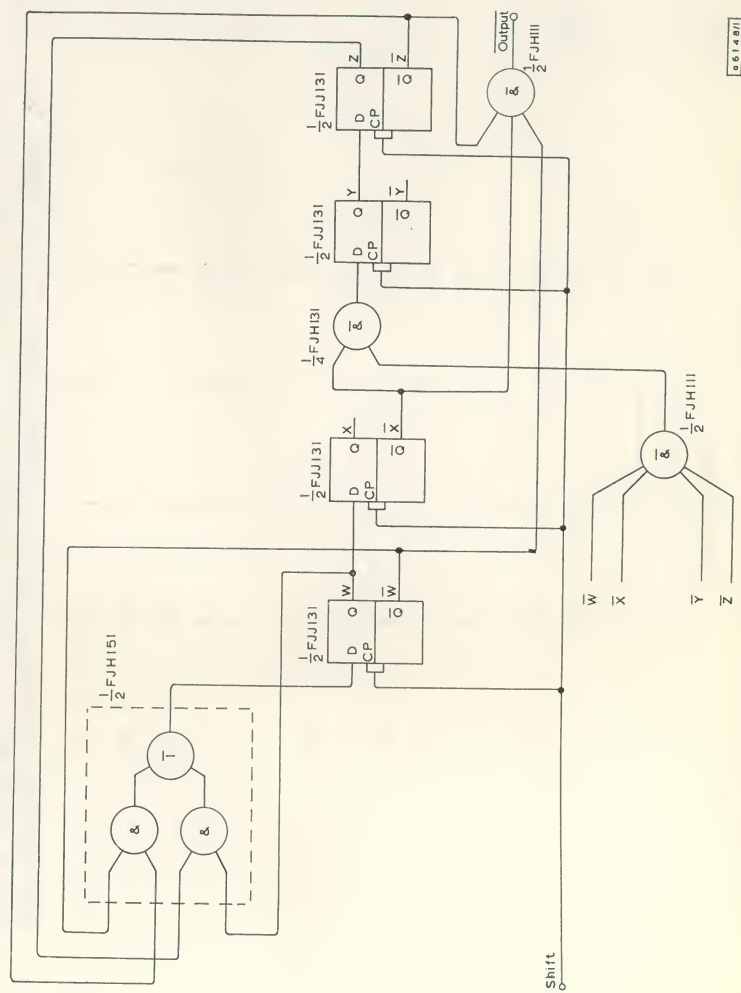


Fig. 107—Alternative four-stage chain code generator with cycle length of fifteen

Truth Table

Z	Y	X	W	F
0	1	0	0	0
1	0	0	0	1
0	0	0	1	1
0	0	1	1	1
0	1	1	1	1
1	1	1	1	0
1	1	0	1	1
1	0	1	0	1
0	1	0	1	1
1	0	1	1	0
0	1	1	0	0
1	1	0	0	1
1	0	0	1	0
0	0	1	0	0

The Boolean expression for the feedback factor, F, is given by
 $F = \bar{W}.Z + W.\bar{Z}$.

CHAIN CODE GENERATOR WITH SHORTENED CYCLE LENGTH

Four stages, cycle length of six

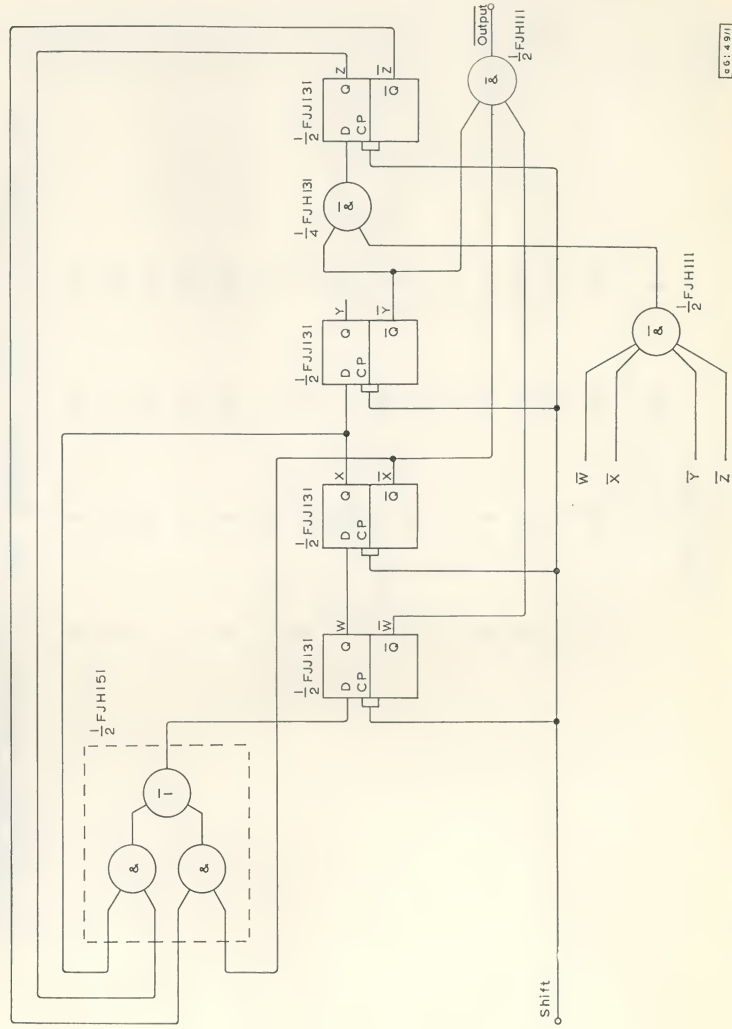


Fig. 108—Example of a chain code generator with cycle length of less than 2^n-1

Truth Table

Z	Y	X	W	F
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
1	0	1	0	0
0	1	0	0	0
1	0	0	0	1

The Boolean expression for the feedback factor, F, is given by

$$F = \bar{X}.Z + X.\bar{Z}.$$

132

The Boolean expression for the feedback factor, F, is given by $F = X.\bar{Z} + \bar{X}.Z$.

SIX-STAGE CHAIN CODE GENERATOR WITH CYCLE LENGTH OF 63

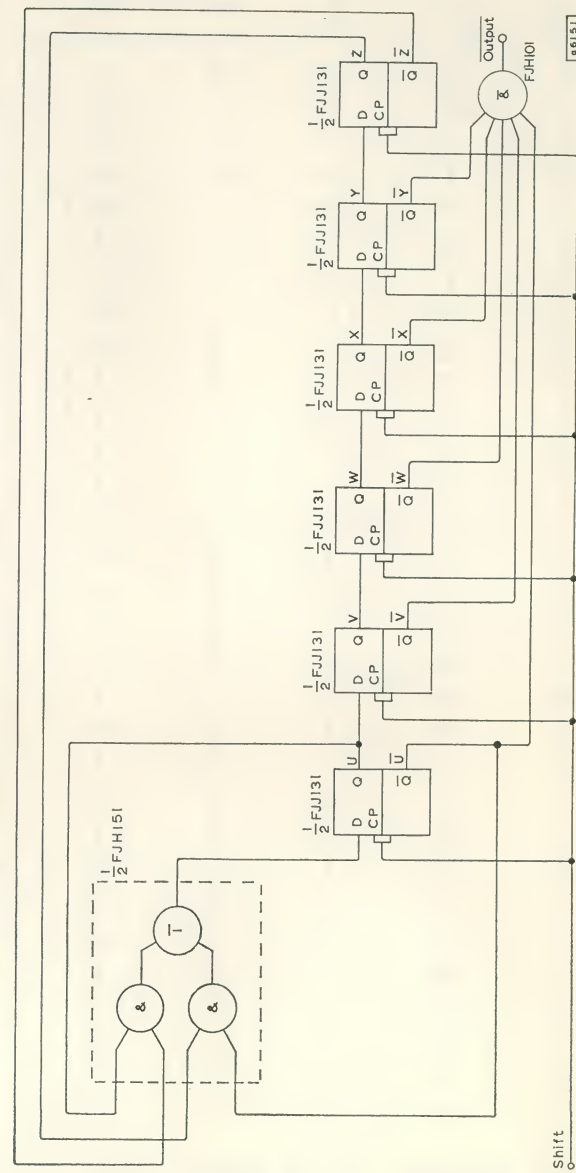


Fig. 110—Six-stage chain code generator with cycle length of 63

Truth Table

Z	Y	X	W	V	U	F
0	0	0	0	0	1	1
0	0	0	0	1	1	1
0	0	0	1	1	1	1
0	0	1	1	1	1	1
0	1	1	1	1	1	1
1	1	1	1	1	0	1
1	1	1	1	0	1	0
1	1	1	0	1	0	1
1	1	0	1	0	1	0
1	0	1	0	1	0	1
0	1	0	1	0	1	1
0	1	0	0	1	1	0
0	1	0	1	1	0	0
0	1	1	0	1	0	1
0	1	1	1	0	1	1
1	0	1	1	1	0	1
1	0	1	1	1	1	0
1	1	0	1	1	0	1
1	1	0	1	0	1	0
1	0	1	0	1	0	0
1	0	1	0	0	1	0
0	1	0	0	1	0	0
0	1	0	0	0	1	0
0	0	1	0	0	1	1
0	0	1	0	0	1	1

(Continued on page 136)

Truth Table

Z	Y	X	W	V	U	F
0	1	0	0	1	1	1
1	0	0	1	1	1	0
0	0	1	1	1	0	0
0	1	1	1	0	0	0
1	1	1	0	0	0	1
1	1	0	0	0	1	0
1	0	0	0	1	0	1
0	0	0	1	0	1	1
0	0	1	0	1	1	1
0	1	0	1	1	1	1
1	0	1	1	1	1	0
0	1	1	1	1	0	0
1	1	1	1	0	0	1
1	1	1	0	0	1	0
1	1	0	0	1	0	1
1	0	0	1	0	1	0
0	0	1	0	1	0	0
0	1	0	1	0	0	0
1	0	1	0	0	0	1
0	1	0	0	0	1	1
1	0	0	0	1	1	0
0	0	0	1	1	0	0
0	0	1	1	0	0	0
0	1	1	0	0	0	0
1	1	0	0	0	0	1
1	0	0	0	0	1	0
0	0	0	0	1	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
1	0	0	0	0	0	1

The Boolean expression for the feedback factor, F, is given by $F = \bar{U}.Z + U.Z$.

SIX-STAGE JOHNSON CODE GENERATOR WITH A CYCLE LENGTH OF TWELVE

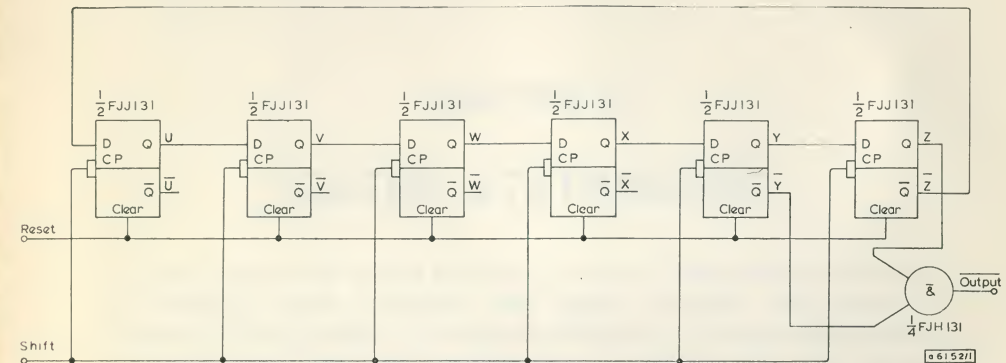


Fig. 111—Six-stage Johnson code generator with cycle length of twelve

Truth Table

Z	Y	X	W	V	U
0	0	0	0	0	0
0	0	0	0	0	1
0	0	0	0	1	1
0	0	0	1	1	1
0	0	1	1	1	1
0	1	1	1	1	1
1	1	1	1	1	1
1	1	1	1	1	0
1	1	1	0	0	0
1	1	0	0	0	0
1	0	0	0	0	0
0	0	0	0	0	0

CHAPTER 12

GATED STATICISERS

A gated staticiser is for use between a source of information which is to be sampled—such as a counter, shift register, or adder—and a store or indicator. The purpose of the gated staticiser is to sample information and hold it until the next sampling time. A signal on the store control line enables information to be transferred from the counter to the staticiser.

A common example of the use of gated staticisers is in counting instruments where the contents of the last count must be displayed while the current count is in progress.

GATED STATICISERS

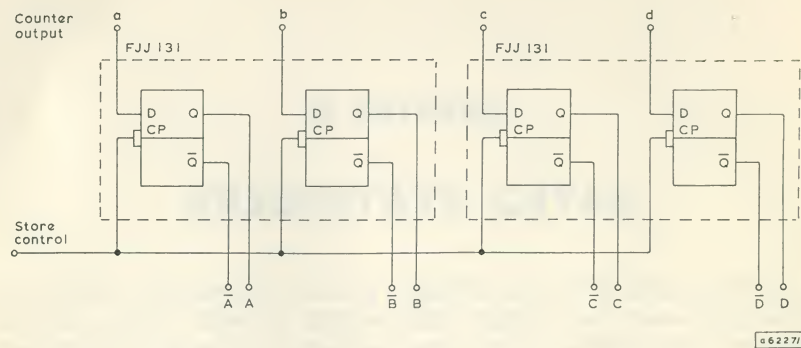


Fig. 112—Gated staticiser using D bistable elements for use between a four-bit counter and a decoder

 


Fig. 113—Block diagram illustrating use of quad D-bistable element as gated staticiser in conjunction with a decade counter and a numerical indicator tube driver

CHAPTER 13

MONOSTABLE CIRCUITS

A monostable circuit is sometimes known as a “one-shot” multivibrator. Its chief function is as a timing circuit because it gives a pulse of any required length when triggered by something less predictable—for example, a manually operated push-button.

THREE-GATE MONOSTABLE CIRCUITS

 


Fig. 114—Three-gate monostable circuit without triggering circuit

 


Fig. 115—Three-gate monostable circuit with triggering circuit

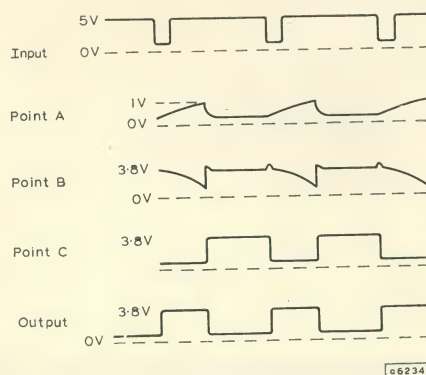


Fig. 116—Waveforms for three-gate monostable circuits

Performance of Three-gate Monostable Circuit

C	Pulse duration
1μF	1.5ms
100nF	140μs
10nF	15μs
1nF	1.4μs
100pF	140ns

The pulse width is independent of frequency down to a duty cycle of 1:1.

The triggering circuit incorporated in Fig. 115 responds to negative-going pulses. For 3V amplitude, the fall rate can be as slow as 0.1μs/V with a triggering capacitor of 100pF. The advantage of this triggering method is that the trigger pulse can be of a longer duration than the output pulse of the monostable circuit.

The stability of the pulse duration despite variations in supply voltage is such that a 10% increase in supply voltage causes the pulse duration to decrease by about 6%. The stability despite variations in temperature is such that an increase of 20°C above room temperature causes the pulse duration to increase by about 3%.

During the time in which the voltage at point C is changing, the noise margin is diminishing. At the instant before the end of the output pulse, the noise margin becomes zero.

CHAPTER 14

MULTIVIBRATORS

A multivibrator is a square-wave oscillator used for generating a continuous supply of pulses. Because multivibrators are used as sources of clock pulses, they are frequently required to have a very high fan-out, making the use of a line-driver gate necessary.

With a basic multivibrator circuit there is the possibility that, if both timing capacitors become charged simultaneously, no oscillation occurs. To overcome this difficulty a self-starter gate may be incorporated.

The stability of the frequency despite variations in supply voltage and temperature is similar to that of the monostable circuits described in Ch. 13.

FOUR-GATE MULTIVIBRATORS

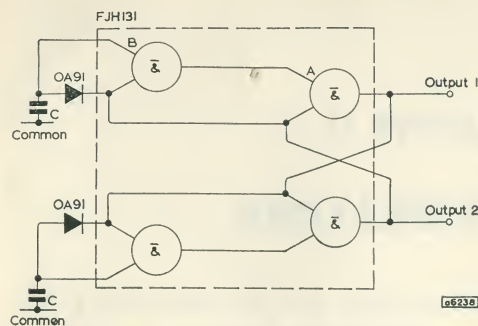


Fig. 117—Four-gate multivibrator

 


Fig. 118—Waveforms for four-gate multivibrator with a value of C of 100nF

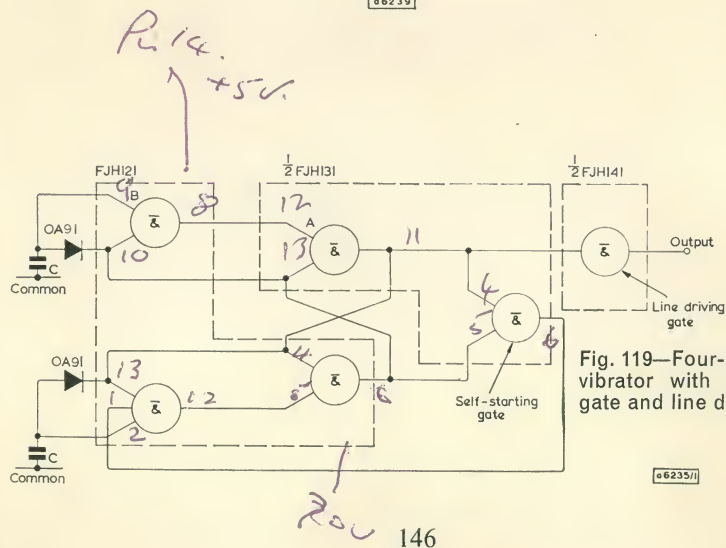


Fig. 119—Four-gate multivibrator with self-starter gate and line driver

Performance

C	Frequency
1 μ F	330Hz
100nF	3.3kHz
10nF	33kHz
1nF	330kHz
100pF	3.3MHz
33pF	10MHz

CHAPTER 15

LEVEL DETECTORS

A level detector, or Schmitt trigger, is a bistable circuit which changes state in accordance with the d.c. input level, producing a fast switching action irrespective of the rate of change of the input voltage. This action is useful for pulse shaping or reforming after the pulse has been degraded by other circuits. Another example of its use is voltage-sensitive switching of relays or lamps where it is essential because of power dissipation problems that the output transistor must operate only in the cut-off or bottomed states.

LEVEL DETECTOR

 


Fig. 120—Level detector using FJY101

 


Fig. 121—Performance of level detector with values of R_1 and R_2 of 56Ω and $3.3k\Omega$ respectively, and a fan-out of 1